

R15

Code No: 124DT

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year II Semester Examinations, May - 2017

SWITCHING THEORY AND LOGIC DESIGN

(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART - A**(25 Marks)**

- 1.a) $AB + A'C + BC = AB + A'C$ represents which theorem. [2]
- b) How do you obtain dual of an expression? [3]
- c) What are don't cares? [2]
- d) Explain the wired logic. [3]
- e) Compare latch and flip flop. [2]
- f) Explain the timing considerations of sequential circuits. [3]
- g) What are the drawbacks of ripple counters? [2]
- h) Explain about state diagram. [3]
- i) List the capabilities of finite state machine. [2]
- j) Explain about ASM chart. [3]

PART - B**(50 Marks)**

- 2.a) Convert the given Gray code number to equivalent binary 00100101110010.
- b) Convert $(A0F9.0EBA98.0DC)_{16}$ to decimal, binary, octal. [5+5]

OR

- 3.a) Simplify the following Boolean expressions using the Boolean theorems.
(i) $(A+B+C)(B'+C) + (A+D)(A'+C)$ (ii) $(A+B)(A+B')(A'+B)$
- b) Why a NAND and NOR gates are known as universal gates? Simulate all the basic Gates. [5+5]
- 4.a) Minimize the following expressions using K-map and realize using NAND Gates.
 $f = \sum m(1, 3, 5, 8, 9, 11, 15) + d(2, 13)$.
- b) Simplify the following boolean function using Tabular method.
 $F(A,B,C,D) = \sum m(0,1,2,5,7,8,9,10,13,15)$ [5+5]

OR

5. With the help of Logic diagram and Truth Table, discuss 8×1 Multiplexer and then realize $f(x,y,z) = \sum m(1,2,4,7)$ using 8×1 MUX as well as using 4×1 MUX. [10]

- 6.a) Explain the operation JK master slave flip flop. Explain its truth table.
b) Explain the realization of SR flip-flop, JK flip-flop using D flip-flop. [5+5]
- OR**
- 7.a) Realize D-FF and T-FF using JK-FF. Draw the logic diagrams with their truth tables.
b) Deduce the design procedure for sequential logic circuits and give the classification of sequential logic circuits. [5+5]
- 8.a) Design and explain a synchronous MOD-12 down-counter using j-k flipflop.
b) Design and explain a 4-bit ring counter using D-flip flops with relevant timing diagrams. [5+5]
- OR**
- 9.a) Design a MOD-10 ripple counter.
b) Design and construct MOD-5 synchronous counter using JK flip flops. [5+5]
- 10.a) What are the capabilities and limitations of finite state machines? Discuss.
b) Explain the procedure for state minimization using merger graph and merger table. [5+5]
- OR**
- 11.a) Differentiate between an ASM chart and a conventional flow chart.
b) Explain in detail the ASM technique of designing a sequential circuit. [5+5]

--ooOoo--