

R16

Code No: 133AQ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, November/December - 2018

ELECTRONIC CIRCUITS

(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**

- 1.a) Write the effect of Distortion in Amplifier circuits. [2]
- b) Illustrate frequency response of BJT Amplifier. [3]
- c) Write the condition for oscillations and its sustenance. [2]
- d) How does negative feedback effect the input and output resistances? [3]
- e) Mention the achievable Maximum Efficiency of Class - A Amplifier. [2]
- f) Write about the concept of Thermal Runway and its counter measures. [3]
- g) What is a negative peak clamper? [2]
- h) Discuss in brief about Clipping at Two Independent Levels. [3]
- i) List the Transistor Switching Times. [2]
- j) Distinguish between bistable, monostable and astable multivibrators. [3]

PART-B**(50 Marks)**

- 2.a) Discuss the variation of A_i , A_v , R_{i_s} and R_o with R_s and R_L in Common Emitter configuration. [5+5]
 - b) Discuss the significance of Miller's theorem in transistor circuit analysis. [5+5]
- OR**
3. Design and explain the circuit diagram of Common Emitter amplifier and then derive an expression for the Voltage gain, current gain, Input Impedance and output Impedance. [10]
 4. Draw the circuit diagram of a current series feedback and derive expressions for Voltage gain, output resistance and input resistance. [10]
- OR**
5. Derive the condition for sustaining the oscillations for a Colpitts Oscillator and also frequency of oscillators. [10]
 - 6.a) Explain the operation of a complementary symmetry class-B power amplifier. [7+3]
 - b) Write the methods to avoid the cross over distortion in power amplifiers circuit. [7+3]
- OR**
- 7.a) Mention about the Phase Inverters and their applications in brief. [5+5]
 - b) Discuss the requirements of heat sink and there types for large signal amplifiers. [5+5]

AG AG AG AG AG AG AG A

- 8.a) Discuss about the practical Clamping using Diode with different inputs.
b) Draw the basic circuit diagram of a DC restorer circuit and explain its operation. [5+5]

OR

AG AG AG AG AG AG AG A

- 9.a) Explain the circuit diagram of an emitter-coupled clipping circuit with its Characteristics.
b) Draw the RC high pass circuit and explain its working with step voltage input. [5+5]

- 10.a) Explain the operation of a diode as a switch and discuss its piece wise linear Characteristics.
b) Write a note on the breakdown Voltage Consideration of Transistor. [5+5]

OR

AG AG AG AG AG AG AG A

11. Draw and explain the operation of Schmitt Trigger with its waveforms and derive the expression for pulse width. [10]

(---oo0oo---

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A

(AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A

AG AG AG AG AG AG AG A