

R16

Code No: 133AB

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B.Tech II Year I Semester Examinations, May/June - 2019****ANALOG ELECTRONICS****(Common to ECE, ETM)****Time: 3 Hours****Max. Marks: 75****Note:** This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

PART- A**(25 Marks)**

- 1.a) What are the types of distortion in amplifiers? [2]
- b) Write the difference between cascade and cascode amplifiers? [3]
- c) Define Gain Bandwidth Product. [2]
- d) What are the elements in the hybrid π model? [3]
- e) Distinguish between enhance mode and depletion mode of MOSFET. [2]
- f) What is folded Cascode amplifier? [3]
- g) What is meant by positive and negative feedback? [2]
- h) What are the conditions for oscillation? [3]
- i) Compare class A and class B amplifier. [2]
- j) Define Q-Factor in tuned amplifiers. [3]

PART-B**(50 Marks)**

2. Draw the h-parameter equivalent circuit for a typical common emitter amplifier and derive expression for A_i , A_v , R_i and R_o . [10]

OR

- 3.a) For any transistor amplifier, Prove that $R_i = (h_i / 1 - h_r A_v)$
- b) Draw the circuit diagram of RC coupled amplifier. Explain the operation and its frequency response. [5+5]

4. Derive the expression for the CE short circuit gain A_i as a function of frequency using hybrid - π model. [10]

OR

- 5.a) In hybrid 'Pi' model of a transistor at high frequencies, show that the g_m is proportional to collector current.

- b) Mention important characteristics of CE amplifier. [5+5]

- 6.a) With the help of a neat diagram explain the operation of an n-channel enhancement type MOSFET.

- b) Explain how you set a Q point in a self- biased JFET. [5+5]

OR

- 7.a) Derive the relation between u and g_m of JFET amplifier.

- b) A JFET has a drain current of 6mA. If $I_{DSS} = 12mA$ and $V_P = 4V$ find:

i) V_{GS} ii) For an n-channel amplifier FET $I_{DSS} = 5.8 mA$, $V_P = -3V$ and $V_{GS} = -2V$ find I_D and g_m .

[5+5]

8.a) An amplifier has a midband gain of 125 and a bandwidth of 250KHz. If 4% negative feedback is introduced, find the new bandwidth and gain.

b) Derive an expression for frequency of oscillations of a RC phase shift oscillators. [5+5]

OR

9.a) What are the advantages and disadvantages of the introduction of negative feedback in amplifiers? Explain.

b) Draw and explain the operation of Colpitt's oscillator. [5+5]

10. Draw the circuit diagram of class B push pull amplifier and explain its operation. Also prove that its conversion efficiency is 78.5%. [10]

OR

11.a) Explain the principle of operation of class-AB power amplifier with a neat sketch.

b) Discuss in detail about frequency response of tuned amplifiers. [5+5]

---0000---

www.FirstRanker.com