

R13

Code No: 126AG

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD
B. Tech III Year II Semester Examinations, May - 2019
COMPUTER METHODS IN POWER SYSTEMS

(Electrical and Electronics Engineering)

Time: 3 hours
Max. Marks: 75
Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10 marks and may have a, b, c as sub questions.

PART - A
(25 Marks)

- 1.a) Define the terms: graphs, tree, co-tree. [2]
- b) Distinguish between branch and node voltage and current. [3]
- c) What is slack Bus? What is its role in load flow solution? [2]
- d) What is acceleration factor? Give its significance. [3]
- e) What is symmetrical component analysis? Explain. [2]
- f) What are the classification line faults and their general behavior? [3]
- g) What is synchronizing power coefficient? Explain. [2]
- h) What are the methods to improve steady state stability? [3]
- i) Give your comment on the system stability with (or) with out considering damper windings. [2]
- j) Give the advantages of auto reclosing and fast acting circuit breaker from the system stability point of view. [3]

PART - B
(50 Marks)

- 2.a) Form the Y_{BUS} for the systems shown in below figure 1 using direct inspection method. Take half line charging susceptance as $j25$.


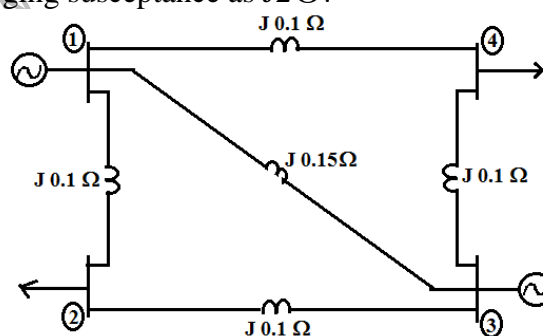


Figure 1

- b) Give the Z_{BUS} building algorithm. [5+5]

OR

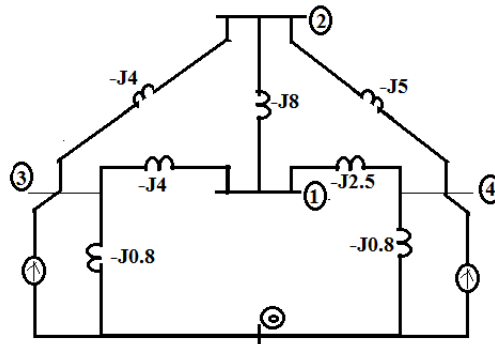- 3.a) Determine the Y_{BUS} for the system shown in below figure 2 using singular transformation method.



(Per unit admittance diagram)

Figure 2

- b) Form the Z_{BUS} for the system shown in below figure 3. [5+5]

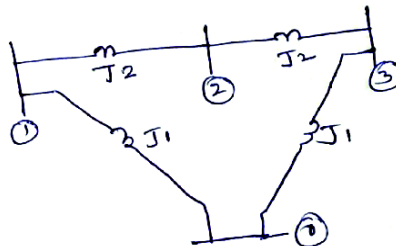


Figure 3

4. Explain the Gauss Seidal Load flow solution method with the help of algorithm and flowchart. Also include the logic for PV buses. [10]

OR

- 5.a) Explain the fast decoupled load flow algorithm. List out all the assumptions made in arriving to it.

- b) Briefly discuss about DC load flow method and its merits and demerits. [5+5]

6. For the system shown in below figure 4 has the following:



Figure 4

Generator: 30 MVA, 13.8 kV, 3 phase alternator has $X_d'' = 15\%$, $X_2 = 15\%$, $X_0 = 5\%$ and $X_n = 2 \Omega$.

Motor: M_1 : 20 MVA, 12.5 kV with $X_d'' = 20\%$, $X_2 = 20\%$, $X_0 = 5\%$ and $X_n = 2 \Omega$.

Motor: M_2 : 10 MVA, 12.5 kV with $X_d'' = 20\%$, $X_2 = 20\%$, $X_0 = 5\%$.

Transformers 1 & 2: 35 MVA, 13.2 Δ / 115 Y with leakage reactance of 10%.

Transformer Line: Total line reactance of 200 Ω . Take the MVA and kV rating in generator circuit as base values.

- a) Obtain the positive, negative and zero sequence networks of the system.

- b) Determine the fault current when a LG fault takes place at point 'p'. Assume the prefault voltage at fault point equal to 1.0 per unit and initial loadings are zero. [10]

OR

- 7.a) Obtain the symmetrical components for the system of unbalanced voltages given by $I_a = 50 \angle 0^\circ$, $I_b = 50 \angle -100^\circ$, $I_c = 50 \angle +125^\circ$
- b) What is short circuit MVA rating of a Bus? Give physical significance of it and explain the role of series reactors in power system.
- c) Derive the expression to determine the LG fault current between phase 'a' and ground using symmetrical component analysis. [10]
- 8.a) Define steady state transient stability of the power system and deduce the necessary condition for the system to be steady state stable is $\frac{dp}{d\delta} > 0$.
- b) Derive the power angle curve for a single machine connected to infinite system through a lossless line having a line reactance of $jX \Omega$. Assume machine impedance is merged into line (figure 5). [5+5]

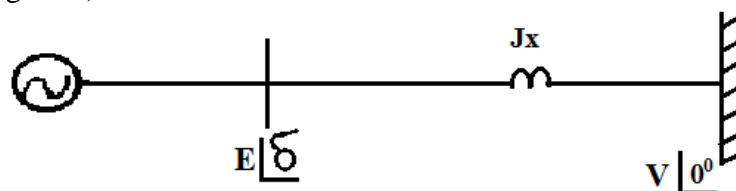


Figure 5

OR

9. For the system shown in below figure 6.

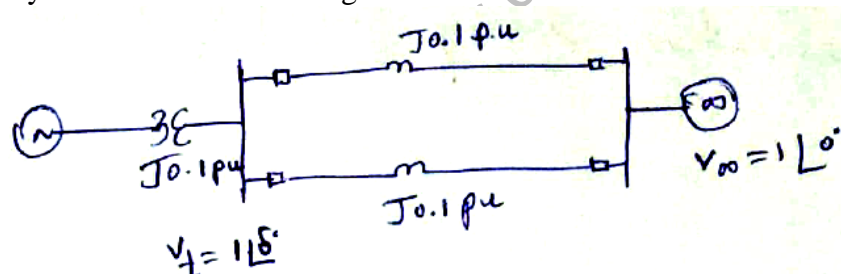


Figure 6

- a) For an initial operating condition $p_m = p_e = 1.0$ pu. Determine the power angle curve of the machine.
- b) For a fault at the mid point of second line, what is the new power angle curve of the machine?
- c) If the fault is cleared by opening the line, determine the post fault power angle curve of the machine. [10]
- 10.a) Briefly explain the concept of determining the transient stability of a SMIB system using equal area criterion.
- b) A SMIB system under steady state delivers 1.0 per unit power to the infinite system and has a power angle equation of $P_e = 2.1 \sin \delta$. Determine the critical clearing angle of the system when a 3 phase fault occurs at the generator system. [5+5]
- OR
11. Explain the step by step procedure to solve the swing equation using point by point method. [10]