

Code No: **R31022/R10****III B.Tech I Semester Supplementary Examinations, November - 2015****ELECTRICAL MEASUREMENTS****(Electrical and Electronics Engineering)****Time: 3 hours****Max. Marks: 75****Answer any FIVE Questions****All Questions carry equal marks**

\*\*\*\*\*

- 1 a) Discuss briefly the essential features of indicating instruments. [7]  
b) Derive the equation for deflecting torque of PMMC instrument when it is spring controlled. [8]
- 2 Derive the expressions for ratio and phase angle error of a potential transformer. State the assumptions made for derivation of these errors. [15]
- 3 a) What is phantom loading? Explain with an example how it is more advantageous than testing with direct loading. [7]  
b) Explain the construction and principle of operation of a dynamometer type Wattmeter. How it can be made to read DC as well as AC? [8]
- 4 a) A basic slide wire potentiometer has a working battery voltage of 3 volts with negligible internal resistance. The resistance of slide wire is  $400\Omega$  and its length is 200 cm. A 200 cm scale is placed along the slide wire. The slide wire has 1 mm scale divisions and it is possible to read upto a division. The instrument is standardized with 1.018 V standard cell with sliding contact at the 101.8 cm mark on scale. Calculate: i) Working current, ii) The resistance of series rheostat, iii) The measurement range and iv) The resolution of the instrument. [7]  
b) Explain with the help of suitable diagrams, how a D.C. Potentiometer can be used for: [8]  
i) Calibration of Voltmeter, ii) Calibration of Wattmeter.
- 5 a) Why is Kelvin's double bridge superior to the Wheat-stone bridge for the purpose of low resistance measurement? [4]  
b) How the difficulties associated with the measurement of very high resistance are over come? [4]  
c) Why is the Voltmeter-Ammeter method unsuitable for the precise measurement of the low resistance? [4]  
d) How the effects of contact resistance and resistance of the connecting leads are eliminated in the measurement of resistance by Kelvin's double bridge? [3]
- 6 a) Explain the working of Hay's bridge for measurement of inductance with a circuit diagram. [7]  
b) A capacitor bushing forms arm AB of a Schering bridge and a standard capacitor of 500 pF capacitance and negligible loss, forms arm AD. Arm BC consists of a non-inductive resistance of  $300\Omega$ . When the bridge is balanced arm CD has a resistance of  $72.6\Omega$  in parallel with a capacitance of  $0.148 \mu\text{F}$ . The supply frequency is 50 Hz. Calculate the capacitance and dielectric loss angle of capacitor. Derive the equations for balance and draw the phasor diagram under conditions of balance. [8]
- 7 a) Discuss any one method of measuring core loss of a magnetic material. [7]  
b) Explain the operating principle of flux meter with a neat sketch. [8]
- 8 Explain the principle of operation of a successive approximation type of Digital voltmeter with a neat block diagram. [15]

-000-

