

Code No: **R31024****R10****Set No. 1****III B.Tech I Semester Supplementary Examinations, May/June - 2015****POWER ELECTRONICS****(Electrical and Electronics Engineering)****Time: 3 hours****Max. Marks: 75****Answer any FIVE Questions****All Questions carry equal marks**

- 1 a) Draw the symbol of a thyristor and list the merits and demerits of thyristors. [7]
b) Define and explain *delay time*, *rise time* and *spread time* of a thyristor. [8]
- 2 Explain in detail the two transistor analogy of an SCR. [15]
- 3 a) What is pulse number of a converter? Explain with an example. [7]
b) What is half wave converter? Derive the expression for an average DC output voltage of a single-phase half wave converter with R load [8]
- 4 A single-phase fully controlled bridge rectifier supplies R load. By assuming the constant output current, find the following performance factors if the supply voltage is 230V and if the firing angle is $\pi/6$ and $R = 5\Omega$. [15]
(i) Average output voltage, (ii) Supply RMS current, (iii) Supply fundamental current, (iv) Fundamental power factor, (v) Input power factor and (vi) Voltage ripple factor.
- 5 a) Explain the advantages of three-phase converters over single-phase converters. [7]
b) Discuss the operation of single-phase dual converter. [8]
- 6 a) What do you mean by ac voltage controller? Give the merits and demerits of it. [7]
b) Give the principle of integral cycle control for a single-phase ac voltage controller. [8]
- 7 With a neat sketch, explain the working principle of type B and type C choppers. [15]
- 8 Calculate the output frequency of a series inverter for the following parameters and find out the attenuation factor: [15]
 $L=10\text{ H}$, $C=0.1\mu\text{F}$, $R=400\Omega$, $T_{\text{off}}=0.2\text{ sec}$

-000-

Code No: **R31024****R10****Set No. 2****III B.Tech I Semester Supplementary Examinations, May/June - 2015****POWER ELECTRONICS****(Electrical and Electronics Engineering)****Time: 3 hours****Max. Marks: 75****Answer any FIVE Questions****All Questions carry equal marks**

- 1 a) Discuss the basic operation of a thyristor and list the different applications of thyristors. [8]
b) Define and explain *reverse recovery time* and *gate recovery time* of a thyristor. [7]
- 2 a) With a neat schematic diagram, explain the UJT firing circuit. [8]
b) SCR with rating of 1200V and 250A are used in a string to handle 5kV and 2kA. Calculate the number of series and parallel units required in case derating factor is i) 0.2 and ii) 0.4 [7]
- 3 a) Define and explain firing angle. [4]
b) Give the classification of phase controlled converters. [6]
c) What are line-commutated converters? Explain. [5]
- 4 a) Give some examples for RL type loads. [5]
b) A single-phase full converter is connected to 230V, 50Hz supply. The load current ' I_0 ' is assumed to be continuous and the turns ratio is unity. Find E_{dc} , E_{rm} , and power factor for a delay angle of $\pi/3$. [10]
- 5 What are dual converters? What are their applications? Explain the operation of a three-phase dual converter. [15]
- 6 a) Give the difference between two SCRs connected in antiparallel and a triac for the same purpose. [7]
b) What is a Triac? Discuss the operation of a Triac with R-L load. [8]
- 7 Derive an expression for output voltage in terms of duty cycle for a step up, step down and step down/up chopper. [15]
- 8 What is a full bridge inverter? Draw the circuit schematic for a single phase full bridge inverter and hence explain its operation. [15]

-000-

Set No. 3

Max. Marks: 75

- 1 a) Draw and discuss static V-I characteristics of a thyristor. [8]
b) Explain the operation of IGBT. Also mention its advantages compared to SCR. [7]
- 2 a) What is the need for snubber circuit? Explain. [7]
b) A 150A SCR is to be connected in parallel with a 200A SCR. The ON state voltage drops of the SCRs is given as 2.0V and 1.9V respectively. Calculate the series resistance that should be connected with each SCR, if the two SCRs have to share the current of 350A in proportion to their ratings. [8]
- 3 With a neat circuit diagram and waveforms, explain the operation of a single-phase half wave converter with RL load. [15]
- 4 With a neat schematic diagram and necessary waveforms, explain the operation of a fully controlled bridge converter with R-L load. [15]
- 5 A three-phase fully controlled bridge rectifier is supplied at 230V/phase and at a frequency of 50Hz. The source inductance $L_s = 5\text{mH}$ and the load current on dc side is constant at 12A. If the load consists of a dc source voltage of 230V having an internal resistance of 0.9Ω , find the following [15]
 - a) Firing angle
 - b) Overlap angle
- 6 a) What are cycloconverters? Explain its purpose. [7]
b) What are different applications of ac voltage controllers? Explain the operation of single-phase ac voltage controller with R-load. [8]
- 7 Explain the working of first quadrant or type A chopper with suitable voltage and current waveforms. Give the complete time domain analysis of type A chopper. [15]
- 8 A single-phase full bridge inverter has a resistive load of $R = 5\Omega$ and the DC input voltage of $E_{dc} = 220\text{V}$. Calculate [15]
 - i) The RMS output voltage at the fundamental frequency denoted by E_1
 - ii) The output power P_0
 - iii) The average and peak currents of each thyristor
 - iv) The peak inverse voltage of each thyristor
 - v) Output voltage at the fundamental frequency

-000-

Set No. 4