

Code No: **R31026****R10****Set No. 1****III B.Tech I Semester Supplementary Examinations, May/June - 2015****LINEAR & DIGITAL IC APPLICATION****(Electrical and Electronics Engineering)****Time: 3 hours****Max. Marks: 75****Answer any FIVE Questions****All Questions carry equal marks**

- 1 a) Sketch a current mirror circuit and explain its operation. Show how a current mirror can be used as a constant current circuit for a differential amplifier. Explain the circuit operation and discuss its effect. [8]
b) Explain the importance of level translator in an op amp. [7]
- 2 a) Why is it necessary to use an external offset voltage compensating network with practical op - amp circuits? [4]
b) Compare and contrast an ideal op - amp and practical op - amp. [6]
c) Define slew rate and what causes it. How is the slew rate measured? [5]
- 3 a) With suitable circuit diagram explain the operation of a triangular wave generator using a comparator and an integrator. [8]
b) Explain the principle of operation of a precision full wave rectifier with waveforms [7]
- 4 a) Draw and explain the operation of Mono stable multivibrator using 555 timer. Derive the expression for time delay. [8]
b) Draw the dc voltage versus phase difference characteristic of balanced modulator phase detector of a PLL indicating all important regions. [7]
- 5 a) Design a first order wide band-reject filter with a higher cut-off frequency of 100 Hz and a lower cut-off frequency of 1 kHz. Calculate the Q of the filter. [8]
b) Sketch the circuit of a R-2R DAC, explain its operation, and calculate the analog output for any given digital input. Explain the performance of R-2R DAC comparing with that of the weighted-resistor DAC. [7]
- 6 a) Write short notes on priority encoder. [8]
b) Explain the logic diagram and functional table of 4 to 1 line multiplexer. [7]
- 7 a) Design and implement a MOD-10 synchronous counter using J-K flip-flops. [8]
b) Draw logical diagram of a 4-bit shift register. Explain how shift-left and shift-right operations are performed. [7]
- 8 a) Give the comparison between PROM, PLA and PAL. [6]
b) Explain the functional behavior of Static RAM cell? Show the internal structure of 8×4 static RAM. [9]

-000-

Code No: R31026

R10**Set No. 2****III B.Tech I Semester Supplementary Examinations, May/June - 2015****LINEAR & DIGITAL IC APPLICATION****(Electrical and Electronics Engineering)****Time: 3 hours****Max. Marks: 75****Answer any FIVE Questions****All Questions carry equal marks**

- 1 a) Explain the classification of ICs according to their method of fabrication. [8]
b) Discuss about dc analysis of Dual input balanced output amplifier. [7]
- 2 a) Define the Op-Amp parameters: i) Input offset Voltage, V_{io} ; ii) Input bias current, I_{io} [8]
With a practical setup explain how these parameters can be measured.
b) Explain frequency compensation techniques used in op-amps. [7]
- 3 a) Draw & discuss the operation of a log amplifier with a circuit diagram. Derive the expression for output voltage. [8]
b) Design a current to voltage converter using Op-amp and explain how it can be used to measure the output of a photocell. [7]
- 4 a) Design an Astable multivibrator using 555 timer for a frequency of 1 kHz and a duty cycle of 70%. Assume $C=0.1\mu f$. [8]
b) Give the block diagram of NE 565 PLL and explain the role of each block. Make circuit connections to track the incoming signal and explain its operation. [7]
- 5 a) Write the advantages of active filter. Explain different configurations of active filter and discuss their merits and demerits. [8]
b) What are servo-tracking A/D converters? Why are they called so? How is it better than counter type A/D converter? [7]
- 6 a) Realize 16 input multiplexer using two 8 input multiplexers. [7]
b) Implement a 4 bit ripple adder using half-adders/full-adders. [8]
- 7 a) Design a modulo-100 counter using two 74×163 binary counters? [8]
b) Design a 4 bit bidirectional shift register using D flip-flops (Use relevant digital ICs). [7]
- 8 a) Describe the difference between PLA & PAL using logic diagrams. [8]
b) With the help of a circuit diagram, explain the read and write operations of a dynamic RAM cell. Differentiate between static RAM and dynamic RAM. [7]

-000-

Code No: **R31026****R10****Set No. 3****III B.Tech I Semester Supplementary Examinations, May/June - 2015****LINEAR & DIGITAL IC APPLICATION****(Electrical and Electronics Engineering)****Time: 3 hours****Max. Marks: 75****Answer any FIVE Questions****All Questions carry equal marks**

- 1 a) What are the three differential amplifier configurations? Compare and contrast these configurations. [8]
b) Explain ac analysis of differential amplifier. [7]
- 2 a) List out the AC characteristics of an op-amp and discuss about them. [8]
b) Define the terms, CMRR and input bias current. Describe the techniques used for the measurement of these parameters. [7]
- 3 a) Draw the circuit diagram of an integrator circuit and explain its functioning with the Input-output wave forms. Derive the output voltage V_0 of an integrator circuit. [8]
b) Design a monostable multivibrator with trigger pulse shaping which will drive a LED ON for 0.5 sec each time it is pulsed. [7]
- 4 a) Draw the internal circuit diagram of a 555 timer IC and explain how does it functions as astable multivibrator. [8]
b) Define the terms 'Lock range' 'Capture range' and 'Pull in time' pertaining to PLL. Derive the relationship between lock range and capture range through a mathematical expression. [7]
- 5 a) Design a second order Butterworth low-pass filter having upper cut-off frequency 2.5KHz. [8]
b) Draw the schematic block diagram of dual-slope A/D converter and explain its operation. Derive expression for its o/p voltage ' V_0 '. [7]
- 6 a) Design a BCD-to-excess-3 code converter with a BCD-to-decimal decoder and OR gates. [8]
b) Draw the logic diagram of a 4-bit ALU and explain. [7]
- 7 a) Design a modulo-16 synchronous binary counter using J-K flip-flops. [8]
b) Design a 8-bit parallel-in and serial-out shift register? Explain the operation of the above shift register with the help of timing waveforms? [7]
- 8 a) Discuss in detail ROM access mechanism with the help of timing waveforms? [8]
b) Explain the internal structure of 64K×1 DRAM. With the help of timing waveforms discuss DRAM access. [7]

-000-

Code No: **R31026****R10****Set No. 4****III B.Tech I Semester Supplementary Examinations, May/June - 2015****LINEAR & DIGITAL IC APPLICATIONS****(Electrical and Electronics Engineering)****Time: 3 hours****Max. Marks: 75****Answer any FIVE Questions****All Questions carry equal marks**

- 1 a) Draw and explain the internal block schematic of an operational amplifier. [8]
b) Explain different methods to increase the input resistance of an op-amp. [7]
- 2 a) Describe non ideal dc characteristics which add error components to the dc output voltage of an op-amp. [8]
b) Explain Pole-zero compensation technique for an op-amp and give its comparison with other compensation techniques. [7]
- 3 a) Explain the operation of an op-amp based monostable multivibrator. [8]
b) Sketch & explain the circuit operation of log and antilog amplifiers. Calculate output voltages for a given input and show how temperature dependence is minimized. [7]
- 4 a) Explain the operation of Schmitt trigger using 555 timer with its circuit diagram. [8]
b) Give the block diagram of NE 565 PLL and explain the role of each block. Explain how PLL is used as FM demodulator? [7]
- 5 a) Explain the operation of an all pass filter with its circuit diagram. Also determine the phase shift Φ between the input and output at $f=2\text{KHz}$. [7]
To obtain a positive phase shift ' Φ ' what modifications are necessary in the circuit?
b) Draw circuit diagram and explain the 4-bit weighted resistor type D/A converter in detail. What are the limitations of weighted resistor type D/A converter? [8]
- 6 a) Distinguish between encoder and a decoder. [4]
b) Draw the circuit of a 3 to 8 decoder and explain its operation. How this can be used as a DEMUX. [6]
c) Design a full-subtractor using 3:8 decoders. [5]
- 7 a) Design a modulo -16 synchronous binary counter using T- flip flops. [8]
b) Design Johnson counter with ten timing signals. [7]
- 8 a) What is a PROM? What are the advantages and disadvantages of using a PROM as a PLD? [8]
b) Explain with suitable diagrams, the structure of a DRAM cell. [7]

-000-