

Code No: R161208

**R16**
**SET - 1**

**I B. Tech II Semester Supplementary Examinations, Nov/Dec - 2017**  
**ELECTRICAL CIRCUIT ANALYSIS – I**  
 (Electrical and Electronics Engineering)


Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
 2. Answering the question in **Part-A** is Compulsory  
 3. Answer any **FOUR** Questions from **Part-B**


**PART –A**

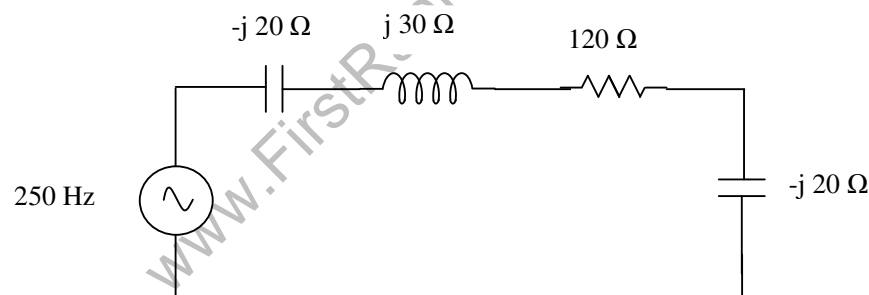1. a) What are dependent Sources and write their symbols. (2M)
- b) Draw a Graph for an electrical network. (2M)
- c) Explain the concept of Mutual Inductance. (2M)
- d) Transform the following sinusoid into Phasor (2M)  
 $I = 5\cos(\omega t - 75^\circ)$ .
- e) What is resonance in an ac series circuit? (2M)
- f) State Reciprocity theorem. (2M)
- g) A series audio circuit is shown in below figure .What is the impedance of the circuit? (2M)



**PART –B**

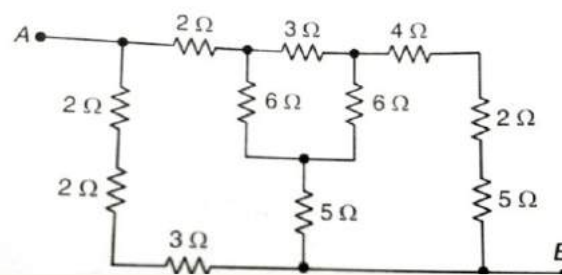2. a) Calculate the effective resistance between the points A and B in the circuit shown in below figure. (7M)



**WWW.MANARESULTS.CO.IN**




Code No: R161208


**R16**

SET - 1

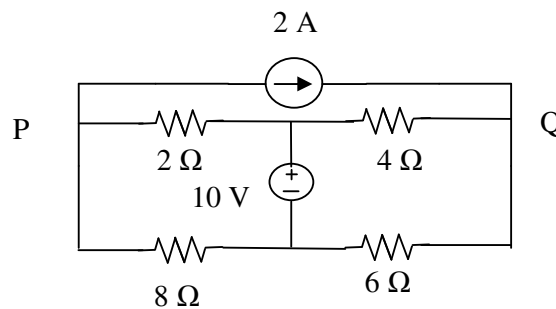
- b) Using nodal analysis, determine the voltage between the points, P and Q shown in below figure. (7M)



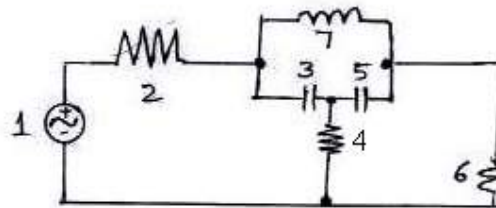3. a) Draw the graph of the network shown in below figure and write down the tie-set matrix. (7M)



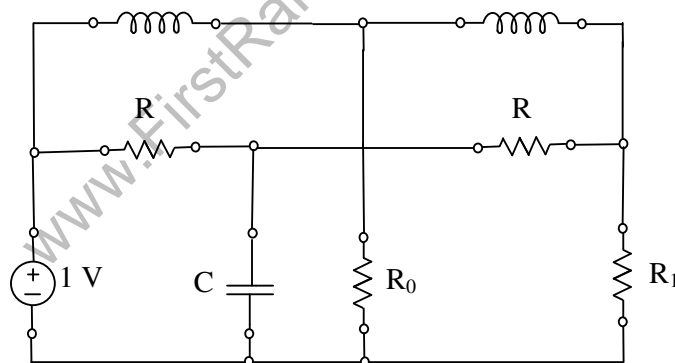- b) Construct the dual of the network shown in below figure. (7M)




4. a) A magnetic circuit consists of an iron ring of mean circumference 90 cm with cross-sectional area of  $10 \text{ cm}^2$  throughout. A current of 2.5 A in the magnetizing coil of 250 turns produce a total flux of 1.2 mwb in the iron. calculate: (7M)
- the flux density in the iron
  - the absolute and relative permeability of iron
  - the reluctance of the circuit.
- b) Two coupled coils have self inductances  $L_1=10\text{mH}$  and  $L_2= 20\text{mH}$ . The coefficient of coupling ( $K$ ) being 0.75 in the air, find voltage in the second coil and the flux of first coil provided the second coil has 500 turns and the circuit current is given by  $i = 2 \sin 314t \text{ A}$ . (7M)

Code No: R161208

**R16**

SET - 1

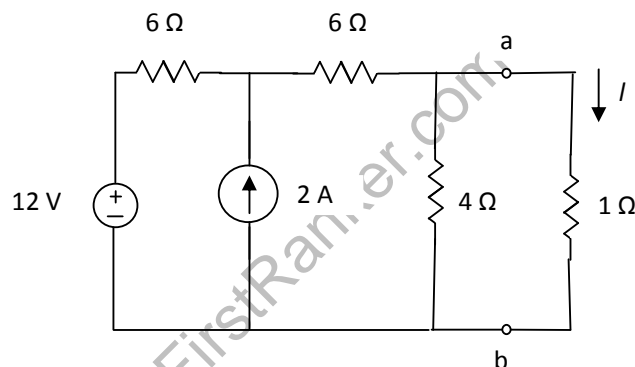5. a) A variable frequency source of  $v = 200$  volt is applied to a series RL circuit having  $R=10\ \Omega$  and  $L=10\text{ mH}$ . Draw Z-locus and I-locus considering sample frequencies  $\omega=0, 500, 1000, 2000$  and  $5000$  rad/sec. (9M)
- b) If voltage  $v = 20 \sin (100t + 40^\circ)$  is applied to a  $60\ \mu\text{F}$  capacitor, calculate the current through the capacitor. (5M)
6. a) At resonance, the current is maximum in a series circuit and minimum in a parallel circuit. Why? (6M)
- b) A resistance of  $12\ \Omega$  and an inductance of  $0.025\text{ H}$  are connected in series across a  $50\text{Hz}$  supply. What values of resistance and inductance when connected in parallel will have the same resultant impedance and pf ? Find the current in each case when the supply voltage is  $230\text{ V}$ . (8M)
7. a) Using Norton's theorem, find the equivalent circuit to the left of the terminals in the circuit of below figure. Then find  $I$ . (7M)



- b) In the network shown in below figure, the  $5\ \Omega$  resistor is changed to  $8\ \Omega$ . Determine the resulting change in current through the  $(3+j4)\ \Omega$  impedance branch using compensation theorem. (7M)

