

Code No: **R32101****R10****Set No. 1****III B.Tech II Semester Supplementary Examinations, April - 2017****DATA ACQUISITION SYSTEMS****(Electronics and Instrumentation Engineering)****Time: 3 hours****Max. Marks: 75**

Answer any FIVE Questions
All Questions carry equal marks

- 1 a) List the Converter Characteristics and explain them.
 b) Discuss the objectives of DAS.
- 2 a) Explain the Principle and design of a Parallel R- 2R DAC.
 b) List the features of DAC.
- 3 a) Explain a ADC that converts Voltage to Time.
 b) Discuss the working of a Dual slope integration.
- 4 a) Explain the function of Programmable non-linear ADCS.
 b) Write the features of Switched capacitor ADCS.
- 5 With neat figure explain the working of a Digitally programmable V/I sources.
- 6 a) Signify the role of ADC in Digital signal processing systems.
 b) Explain the functioning of Electronic weighing machines and what is the role of ADC.
- 7 Explain the Interfacing of DACS to a μP
- 8 Write explanatory notes on
 - a) Error budget analysis of DAS
 - b) Error reduction in DAS
