

Code No: RT22041

**R13****SET - 1**

**II B. Tech II Semester Supplementary Examinations, November - 2018**  
**ELECTRONICS CIRCUIT ANALYSIS**  
(Com. to ECE, EIE)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)  
2. Answer **ALL** the question in **Part-A**  
3. Answer any **THREE** Questions from **Part-B**

**PART -A**

1. a) Explain frequency stability of an oscillator (4M)
- b) Draw and explain about crystal based oscillator. (4M)
- c) What are the characteristics of negative feedback amplifiers (4M)
- d) Define rise time and derive an expression for it. (4M)
- e) Define noise and indicate various types of noises in amplifiers. (3M)
- f) Classify different types of distortions possible in amplifiers. (3M)

**PART -B**

2. a) Draw the equivalent circuit of a common source amplifier at high frequencies. (8M)  
Derive the expression for voltage gain, input and output resistances.
- b) A common drain amplifier uses a MOSFET with the following parameters (8M)  
 $g_m = 2.5\text{mA/V}$ ,  $r_d = 60\text{kohms}$ ,  $C_{gs} = 4\text{pF}$ ,  $C_{ds} = 2\text{pF}$ ,  $C_{gd} = 3\text{pF}$ . The value of  $R_s = 100\text{K ohms}$ . The amplifier operates at  $30\text{KHz}$ . Find Voltage gain, input resistance, output resistance and input capacitance.
3. a) Derive the expressions for voltage gain, current gain, input and output resistances (8M)  
of a Darlington pair.
- b) Draw the circuit diagram of a two stage FET based RC coupled amplifier and (8M)  
derive an expression for voltage gain, input and output resistances.
4. a) A Common source FET amplifier has a load resistance of  $600\text{kOhms}$ . The ac drain (8M)  
resistance of the device is  $150\text{kohms}$  and the transconductance is  $0.75\text{mA/V}^{-1}$ .  
Calculate the voltage gain of the amplifier.
- b) Discuss quantitatively the effect of mixing on input resistance. (8M)
5. a) Derive the frequency of oscillation of Colpitt's oscillator? What are the limitations (8M)  
of this oscillator?
- b) State and explain the Barkhausen criterion in sinusoidal oscillators. (8M)
6. a) What is a cross over distortion in power amplifier and suggest a remedy for it. (8M)
- b) Derive the expression for Maximum efficiency and working of transformer (8M)  
coupled Class Amplifier
7. a) With necessary diagram and explanation derive the expression for efficiency of a (8M)  
class C tuned amplifier.
- b) Explain various types of coupling of transformer used in double tuned amplifiers (8M)  
with necessary diagrams