

Code No: R22023

R10
SET - 1
II B. Tech II Semester Supplementary Examinations, April-2018
SWITCHING THEORY AND LOGIC DESIGN

(Com. to EEE, ECE, ECC, BME, EIE)

Time: 3 hours

Max. Marks: 75

Answer any **FIVE** Questions
 All Questions carry **Equal** Marks
 ~~~~~

1. a) Subtract the following numbers using 2's and 1's complement [8M]  
 (i)  $5250 - 321$  (ii)  $753 - 864$   
 (iii)  $3570 - 2100$  (iv)  $20 - 1000$   
 b) Explain about weighted and non-weighted codes [7M]
2. a) Simplify the following Boolean expressions to a minimum number of literals [8M]  
 i)  $ABC + A'B + ABC'$   
 ii)  $x'yz + xz$   
 iii)  $(x + y)'(x' + y')$   
 b) Implement the following function with NAND gates  $F(x, y) = \Sigma(0, 3)$  [7M]
3. a) Simplify the following using QM Tabular Method [7M]  
 $F(A, B, C, D, E) = \Sigma(0, 2, 4, 6, 9, 11, 13, 15, 17, 21, 25, 27, 2, 31)$   
 b) Minimize the given 5 variable function using K-map method [8M]  
 $f = \Sigma(3, 4, 9, 10, 11, 12, 18, 20, 21, 22, 23, 25, 26, 30)$
4. a) Draw and explain about BCD adder circuit Excess3 adder circuit [7M]  
 b) Draw the logic diagram 4-bit binary adder-subtractor circuit and explain [8M]
5. a) Implement the following Boolean function with a multiplexer [8M]  
 (a)  $F(A, B, C, D) = \Sigma(1, 2, 5, 8, 6, 10, 12, 14)$   
 (b)  $F(A, B, C, D) = \Sigma(1, 2, 5, 6, 12)$   
 b) What is necessity of priority encoder? Explain about 8 to 3 priority encoder. [7M]
6. a) Write the difference between PROM, PLA. [5M]  
 b) A combinational circuit is defined by the functions [10M]  
 $F_1(A, B, C) = \Sigma(3, 5, 6, 7)$   
 $F_2(A, B, C) = \Sigma(0, 2, 4, 7)$   
 Implement the circuit with a PLA having 3 inputs, four product terms and two output
7. a) What is flip flop? Explain about JK flip flop. [8M]  
 b) Explain about universal shift register [7M]
8. a) What is Finite state machine and explain its capabilities [7M]  
 b) Draw a state diagrams of a sequence detector which can detect 011 [8M]