

Code No: RT31044

**R13****SET - 1****III B. Tech I Semester Supplementary Examinations, October/November - 2018****DIGITAL SYSTEM DESIGN & DIGITAL IC APPLICATIONS**

(Common to Electronics Computer Engineering and Electronics Instrumentation Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answering the question in **Part-A** is compulsory3. Answer any **THREE** Questions from **Part-B****PART -A**

- 1 a) Explain about data objects in VHDL. [3M]
- b) Discuss about Technology Libraries. [4M]
- c) Explain briefly Static RAM Internal structure. [4M]
- d) Explain about CMOS steady state electrical behavior. [4M]
- e) Explain the significance of Dual Priority encoder. [4M]
- f) Compare latches and flip flops. [3M]

**PART -B**

- 2 a) Explain the Packages and Libraries of VHDL? [8M]
- b) Compare and contrast between VHDL and Verilog HDL. [8M]
- 3 a) Explain why place and route tools are used in VHDL with the help of data flow diagram. [8M]
- b) Explain in detail about Post Layout Timing Simulation. [8M]
- 4 a) Explain the internal structure of PROM and list its advantages. [8M]
- b) Describe DRAM with an appropriate diagram and explain about its timings. [8M]
- 5 a) Explain dynamic electrical behavior of a CMOS. [8M]
- b) What are the salient features of ECL? and explain its internal structure [8M]
- 6 a) Write the VHDL code for 16 bit barrel shifter. [8M]
- b) Design a 4 bit carry look ahead adder using gates and write the VHDL code for it. [8M]
- 7 a) Write a VHDL program to design a modulo-8 counter. [8M]
- b) Explain in detail about the working of Johnson Counter using 74 LS194. [8M]

\*\*\*\*\*