

Code No: R1631024

R16**SET - 1****III B. Tech I Semester Regular Examinations, October/November - 2018****PULSE AND DIGITAL CIRCUITS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answer **ALL** the question in **Part-A**3. Answer any **FOUR** Questions from **Part-B****PART -A**

1. a) What is meant by linear wave shaping? [2M]
- b) Write the difference between comparator and clipping circuit. [2M]
- c) Write short notes on piece-wise linear diode characteristics. [3M]
- d) What is meant by quasi stable state? [2M]
- e) What is meant by sweep time and restoration time? [3M]
- f) What is Pedestal? Explain. [2M]

PART -B

2. a) A square wave whose peak to peak amplitude is 2 V extends ± 1 V with respect to ground. The duration of the positive section is 0.1 s and that of the negative section is 0.2 s. if this waveform is impressed upon an RC integrating circuit whose time constant is 0.2 s, what are the steady-state maximum and minimum values of the output waveform? [7M]
- b) Explain the response of High-pass RC circuit for square wave input. [7M]
3. a) Draw the circuit diagram of emitter coupled clipper and explain its operation. [7M]
- b) Design a diode clamper circuit to clamp the positive peaks of the input signal at zero level. The frequency of the input voltage is 750 Hz. [7M]
4. a) Explain about diode forward recovery time and reverse recovery time. [7M]
- b) Silicon transistors with $h_{FE}(\text{min}) = 20$ are available. If $V_{CC} = V_{BB} = 10$ V, design the bistable multivibrator. [7M]
5. a) Design a collector coupled one shot with a gate width of 3 ms, using n-p-n transistors. [7M]
- b) Draw the circuit diagram of collector coupled astable multivibrator and derive the expression for frequency of oscillations. [7M]
6. a) Draw the exponential sweep circuit and derive the expression for transmission error. [7M]
- b) Explain the basic principles behind Bootstrap time base generator. [7M]
7. a) Draw the circuit diagram of two input Diode OR gate and explain it. [7M]
- b) Explain the operation of six diode sampling gate. [7M]

Code No: R1631024

R16**SET - 2****III B. Tech I Semester Regular Examinations, October/November - 2018****PULSE AND DIGITAL CIRCUITS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answer **ALL** the question in **Part-A**3. Answer any **FOUR** Questions from **Part-B**

~~~~~

**PART -A**

1. a) What is an attenuator? [2M]
- b) What is meant by positive clamping and negative clamping? [2M]
- c) Write the applications of Schmitt trigger. [3M]
- d) Define astable multivibrator. [2M]
- e) Define transmission error. [2M]
- f) Why sampling gates are called linear gates? [3M]

**PART -B**

2. a) A pulse is applied to low-pass RC circuit. Prove that area under the pulse is same as area under the output waveform across the capacitor. [7M]
- b) Explain the response of High-pass RC circuit for step input. [7M]
3. a) Explain clipping at two independent levels using diodes. [7M]
- b) State and explain clamping circuit theorem. [7M]
4. a) Discuss about breakdown voltages of a transistor. [7M]
- b) Design a bistable multivibrator to meet the following specifications: [7M]  
 $V_{CC} = V_{BB} = 12\text{ V}$ ,  $I_{C(sat)} = 6\text{ mA}$ ,  $h_{FE}(\text{min}) = 25$  and maximum triggering frequency = 25 kHz.
5. a) Derive the expression for gate width of a monostable multivibrator neglecting the reverse saturation current  $I_{CBO}$ . [7M]
- b) Find the ratio  $V_{CC}/V$ , if a voltage to frequency convertor generates oscillations of frequency twice of that when  $V = V_{CC}$ . [7M]
6. a) What is meant by time base signal? What are the general features of time base signal? Explain. [7M]
- b) Explain about transistor miller time base generator. [7M]
7. a) Give the comparison of various logic families. [7M]
- b) Discuss about reduction of pedestal in sampling gates. [7M]

\*\*\*\*\*

Code No: R1631024

**R16****SET - 3****III B. Tech I Semester Regular Examinations, October/November - 2018****PULSE AND DIGITAL CIRCUITS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answer **ALL** the question in **Part-A**3. Answer any **FOUR** Questions from **Part-B**

~~~~~

PART -A

1.
 - a) When does high pass circuit act as a differentiator? [2M]
 - b) What is the difference between clipping and clamping? [2M]
 - c) Define delay time and storage time. [2M]
 - d) Find the period of output and the frequency of oscillation of an astable multivibrator with $R_1 = R_2 = 25 \text{ k}\Omega$ and $C_1 = C_2 = 0.2 \mu\text{F}$. [3M]
 - e) Define displacement error. [2M]
 - f) Write the difference between sampling gate and logic gate. [3M]

PART -B

2.
 - a) Explain the response of Low-pass RC circuit for exponential input. [7M]
 - b) Draw the circuit diagram of compensated attenuator and explain it. [7M]
3.
 - a) Draw the circuit of transistor clipper and explain its operation. [7M]
 - b) Design a diode clamper to restore a dc level of +5 V to an input signal of peak-to-peak value 15 V. Assume the drop across the diode is 0.7 V and the signal frequency is 1 kHz. [7M]
4.
 - a) Explain about design of transistor switch. [7M]
 - b) Explain the operation of Schmitt trigger. [7M]
5.
 - a) Draw the circuit diagram of collector coupled mono stable multivibrator and explain its operation. [7M]
 - b) Design an astable multivibrator to generate a square wave of 1 kHz. [7M]
6.
 - a) Explain the basic principles behind miller time base generator. [7M]
 - b) Discuss about the transistor bootstrap time base generator. [7M]
7.
 - a) Draw the diode logic AND circuit and explain it. [7M]
 - b) Explain the operation of four diode sampling gate. [7M]

Code No: R1631024

R16**SET - 4****III B. Tech I Semester Regular Examinations, October/November - 2018****PULSE AND DIGITAL CIRCUITS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answer **ALL** the question in **Part-A**3. Answer any **FOUR** Questions from **Part-B****PART -A**

1. a) Define the term 'rise time'. [2M]
- b) List out the some applications of voltage comparator. [3M]
- c) What is meant by triggering of binary circuit? [2M]
- d) Why monostable multivibrator also called gating circuit? [2M]
- e) What is meant by voltage time base generator? [2M]
- f) Write the some applications of sampling gates. [3M]

PART -B

2. a) Explain the response of High-pass RC circuit for sinusoidal input. [7M]
- b) Explain the response of series RLC circuit for step input. [7M]
3. a) Draw the basic circuit of diode clipper and explain its operation with the help of transfer characteristics. [7M]
- b) Explain the operation of negative clamping circuit. [7M]
4. a) For a common emitter circuit, $V_{CC} = 15\text{ V}$, $R_C = 1.5\text{ k}\Omega$ and $I_B = 0.3\text{ mA}$. [7M]
(i) Determine the $h_{FE}(\text{min})$ for the saturation to occur.
(ii) If the R_C is changed to $500\text{ }\Omega$, will the transistor be saturated?
b) Design a Schmitt trigger circuit to have $V_{CC} = 12\text{ V}$, $UTP = 6\text{ V}$, $LTP = 3\text{ V}$, using silicon transistors with $h_{FE}(\text{min}) = 60$. [7M]
5. a) Calculate the component values of a monostable multivibrator developing an output pulse of $500\text{ }\mu\text{s}$ duration. Assume $h_{FE}(\text{min}) = 25$, $I_{CE}(\text{sat}) = 5\text{ mA}$, $V_{CC} = 10\text{ V}$, and $V_{BB} = -4\text{ V}$. [7M]
- b) Explain how an astable multivibrator can be used as a voltage to frequency convertor. [7M]
6. a) With necessary waveforms, explain the operation of UJT Relaxation oscillator. [7M]
- b) What are the different methods to generate time base waveforms? Explain. [7M]
7. a) Draw the circuit diagram of TTL NAND gate and explain it. [7M]
- b) Explain the basic principle behind sampling gate. [7M]
