

www.FirstRanker.com

www.FirstRanker.com

Code No: RT31026



SET - 1

III B. Tech I Semester Supplementary Examinations, May -2018 LINEAR & DIGITAL IC APPLICATIONS

(Electrical and Electronics Engineering)

Time: 3 hours

1

Max. Marks: 70

[4M]

[3M]

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**) 2. Answering the question in **Part-A** is compulsory

3. Answer any **THREE** Questions from **Part-B**

PART –A

a)	List the advantages of ICs over discrete components?	[3M]
b)	Define input offset current and input offset voltage	[4M]

c) Give the important features of an instrumentation amplifier. [4M]

- d) Define capture range and lock range?
- e) Draw the circuit of first order active filter.
- f) Compare successive approximation ADC with dual slope ADC. [4M]

PART -B

- 2 a) What is a differential amplifier? Mention the classification of differential amplifier [8M] with neat diagrams.
 - b) Explain ac analysis of dual input balanced output differential amplifier configuration. [8M]
- 3 a) What is an operational amplifier? Give its symbol and also draw its electrical [8M] equivalent circuit.
 - b) An op-amp has a slew rate of 2V/µs. What is the maximum frequency of an output [8M] sinusoid of peak value 5V at which the distortion sets in due to the slew rate limitation?
- 4 a) With a neat sketch explain the instrumentation amplifier [8M]
 - b) Draw the circuit of a voltage to current converter if the load is i) floating and [8M] ii) Grounded. Are there any limitations as the size of the load when grounded?
- 5 a) Draw the block diagram of NE/SE565 PLL and explain the operation with the help of [8M] waveforms.
 - b) What is meant by VCO? Explain in detail and state the applications of VCO? [8M]
- 6 a) Plot and explain frequency response of [8M] i) Low pass Butter worth filter ii) High pass filter iii) Band pass filter iv) Band Reject filter
 - b) Design a second order Low Pass Filter at a high cut off frequency of 2 KHz. Draw the [8M] frequency response and the circuit with all components.

7 a) Compare different types of A-D converters [8M]

b) Find the voltage at all nodes 0, 1, 2 ... and at the output of a 5-bit R-2R ladder DAC. [8M] The LSB is 1 and all other bits are equal to '0'. Assume $V_R = -10V$ and $R = 10 \text{ k}\Omega$

www.FirstRanker.com