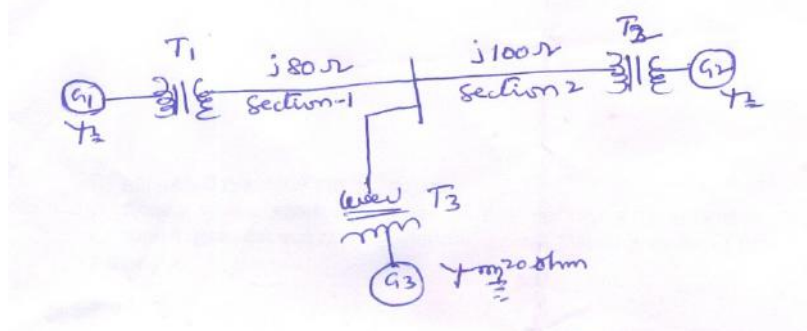


Code No: **R32022**
R10
Set No. 1
III B.Tech II Semester Supplementary Examinations, November - 2018
POWER SYSTEM ANALYSIS

(Electrical and Electronics Engineering)

Time: 3 hours
Max. Marks: 75
Answer any FIVE Questions
All Questions carry equal marks

- 1 The single line diagram of an unloaded power system is show in below figure. [15M]
 The ratings of the generators and transformers as follows:
 $G1 = 100 \text{ MVA}, 26 \text{ kV}, X'' = 10\%$
 $G2 = 50 \text{ MVA}, 13 \text{ kV}, X'' = 15\%$
 $G3 = 75 \text{ MVA}, 12.6 \text{ kV}, X'' = 20\%$
 $T1 = 100 \text{ MVA}, 220/25 \text{ kV}, X = 10\%$
 $T2 = 3 \text{ single phase units each rated at } 20 \text{ MVA}, 127/13 \text{ kV}, X = 10\%$
 $T3 = 50 \text{ MVA}, 220/12 \text{ kV}, X = 10\%$
 Draw the reactance diagram using the base values of generator G1.



- 2 a) What is the necessity of power flow studies in power system studies [8M]
 b) Explain the various types of buses in power systems [7M]
- 3 a) What are the merits and demerits of N-R method over G-S method [8M]
 b) Write an algorithm for fast decoupled load flow method [7M]
- 4 Build the Z_{Bus} using algorithm for a power system whose element data is given [15M]
 in the following table:

Element No.	Connected between bus No.	Self reactance (p.u)
1	1-2	0.1
2	1-3	0.15
3	2-3	0.3
4	2-3	0.1

Set No. 1

- * * * * *