

Code No: QT41048

R13**Set No. 1**

IV B.Tech I Semester Supplementary Examinations, February/March - 2018

DIGITAL IC DESIGN

(Electronics and Communications Engineering)

Time: 3 hours

Max. Marks: 70

*Question paper consists of Part-A and Part-B**Answer ALL sub questions from Part-A**Answer any THREE questions from Part-B*

PART-A (22 Marks)

1. a) Define Inverter threshold voltage. [4]
- b) Explain General circuit structure of an nMOS inverter. [4]
- c) Calculate the W/L ratio of the series connected transistors. [4]
- d) Discuss about 2 address bits row detector. [4]
- e) What is a crosstalk? Explain. [3]
- f) State the advantages of Polysilicon Interconnect. [3]

PART-B (3x16 = 48 Marks)

2. a) Explain necessary theorems of transistor equivalency [8]
- b) Derive the expression for gain, input resistance, output resistance of pseudo NMOS inverter. [8]
3. a) Draw and explain the operation of CMOS Transmission gate. [8]
- b) Derive the expression for V_{OH} and V_{OL} for two input NOR gate [8]
4. a) Draw CMOS AOI realization of the JK latch and explain its operation. [8]
- b) Discuss how a D Latch can be realized using CMOS. [8]
5. a) Explain Domino CMOS Logic gate operation. [8]
- b) Discuss the charge-sharing problems in VLSI circuits. Explain various circuit techniques used in domino CMOS circuits for solving charge-sharing problems [8]
6. a) Explain about capacitive interconnect. [8]
- b) Estimate the capacitance to ground per unit length for a polysilicon interconnect, 0.25 micro meter wide and 0.25 micrometer thick, on a 0.5 micro meter thick layer of silicon dioxide (relative permittivity = 3.9). [8]
7. a) Draw circuit diagrams of the row decoder and the column decoder for an EPROM with 4 rows and 2 columns. Use nMOS technology. Develop formulas for the row and column delays in the EPROM. Define any terms in your formulas which are not obvious. [12]
- b) Define memory and give a classification. [4]