

Code No: RT41041

R13**Set No. 1**

IV B.Tech I Semester Regular/Supplementary Examinations, Oct/Nov - 2018

VLSI DESIGN**(Common to Electronics and Communication Engineering and Electronics and Instrumentation Engineering)**

Time: 3 hours

Max. Marks: 70

*Question paper consists of Part-A and Part-B**Answer ALL sub questions from Part-A**Answer any THREE questions from Part-B*

PART-A (22 Marks)

1. a) Compare CMOS, Bipolar, BiCMOS technologies? [4]
- b) Write a note on the general observation about design rules. [3]
- c) Explain the criteria for choice of layers. [4]
- d) Draw the typical architecture of PLA. [3]
- e) Write a short note on SoC Design. [4]
- f) List the applications of FPGA. [4]

PART-B (3x16 = 48 Marks)

2. a) What are the steps involved in the nMOS fabrication? Explain with neat sketches. [8]
- b) Derive the relationship between drain to source current I_{ds} verses drain to source voltage V_{ds} in non-saturated and saturated region. [8]
3. a) What is a stick diagram? Draw the stick diagram and layout for a CMOS inverter. [8]
- b) Explain about double poly CMOS rules. [8]
4. a) Explain the concept of sheet resistance and apply it to compute the ON resistance (V_{DD} to GND) of an NMOS inverter having pull up to pull down ratio of 4:1, If n channel resistance is $R_{sn} = 104 \Omega$ per square. [8]
- b) What is inverter delay? How delay is calculated to for multiple stages? [8]
5. a) Explain switch logic and its arrangements? And also explain properties of transmission gate. [8]
- b) Discuss the general arrangement of a 4-bit arithmetic process. [8]
6. a) Explain the importance of package selection. [8]
- b) Explain the importance of design for testability. [8]
7. a) Explain about building block architecture of FPGA. [8]
- b) Explain the design flow using FPGA. [8]

Code No: **RT41041****R13****Set No. 2****IV B.Tech I Semester Regular/Supplementary Examinations, Oct/Nov - 2018****VLSI DESIGN****(Common to Electronics and Communication Engineering and Electronics and Instrumentation Engineering)****Time: 3 hours****Max. Marks: 70***Question paper consists of Part-A and Part-B**Answer ALL sub questions from Part-A**Answer any THREE questions from Part-B************PART-A (22 Marks)**

1. a) Define threshold voltage of a MOS device and explain its significance. [4]
- b) Explain how stick diagrams can be used for layout diagrams. [3]
- c) Write short notes on area capacitances of layers. [4]
- d) Explain a four line Gray code to Binary code converter. [4]
- e) Write a short note on mixed signal design. [3]
- f) List out the steps in FPGA design flow. [4]

PART-B (3x16 = 48 Marks)

2. a) Explain the processing steps used in IC fabrication process. [8]
- b) Derive the expression for the ratio between $Z_{p,u}$ and $Z_{p,d}$ if an nMOS inverter is to be driven from another nMOS inverter. [8]
3. a) Design a stick diagram for inverter using CMOS. [8]
- b) Design a layout diagram for CMOS 3-input NAND gate. [8]
4. a) Explain scaling of MOS circuits. Give merits and demerits of scaling. [8]
- b) Describe three sources of wiring capacitances. Explain the effect of wiring capacitance on the performance of a VLSI circuit. [8]
5. a) Discuss about Two-phase clocking in detail. [8]
- b) With an example, Explain about system design. [8]
6. a) Discuss the VLSI design issues and design trends. [8]
- b) Explain the ASIC design flow. [8]
7. a) Write the VHDL code to implement stack. [8]
- b) Explain the architectural features of FPGA. [8]

Code No: **RT41041****R13****Set No. 3****IV B.Tech I Semester Regular/Supplementary Examinations, Oct/Nov - 2018****VLSI DESIGN****(Common to Electronics and Communication Engineering and Electronics and Instrumentation Engineering)****Time: 3 hours****Max. Marks: 70***Question paper consists of Part-A and Part-B**Answer ALL sub questions from Part-A**Answer any THREE questions from Part-B************PART-A (22 Marks)**

1. a) Define the terms SSI, MSI, LSI and VLSI. [4]
- b) Define stick diagram and layout diagram. [3]
- c) Draw and explain fan-in and fan-out characteristics of CMOS design. [3]
- d) Write short notes on switch logic and its arrangements. [4]
- e) Draw the ASIC design flow. [4]
- f) Explain the functions of LUT based logic block. [4]

PART-B (3x16 = 48 Marks)

2. a) With neat sketches explain BICMOS fabrication in an n-well process. [8]
- b) Explain and derive the expressions for MOS transistor parameters g_m , g_{ds} and ω_0 . [8]
3. a) Design a layout for CMOS 2-input NOR gate. [8]
- b) Write a short note on $2\mu\text{m}$ Double Metal, Double Poly, CMOS/BiCMOS rules. [8]
4. a) Explain constituents of wiring capacitance. [8]
- b) What are the limits on logic levels and supply voltage due to noise in scaling? [8]
5. a) Explain bus arbitration logic for n-line bus structured design approach. [8]
- b) Realize the 2-i/p NOR gate using NMOS, PMOS and CMOS technologies. [8]
6. a) Discuss about design for testability in VLSI design. [8]
- b) Draw and explain the FPGA design flow. [8]
7. a) Explain implementation of queue using VHDL [8]
- b) Write the VHDL code to implement four bit shift register. [8]

Code No: RT41041

R13**Set No. 4****IV B.Tech I Semester Regular/Supplementary Examinations, Oct/Nov - 2018****VLSI DESIGN****(Common to Electronics and Communication Engineering and Electronics and Instrumentation Engineering)****Time: 3 hours****Max. Marks: 70***Question paper consists of Part-A and Part-B**Answer ALL sub questions from Part-A**Answer any THREE questions from Part-B************PART-A (22 Marks)**

1. a) Explain the Latch-up effect in CMOS circuits with suitable diagrams. [4]
- b) Draw the circuit diagram for CMOS two-input NOR gate. [3]
- c) Write short notes on realization of gates using CMOS technology. [4]
- d) Explain a four-bit dynamic shift register. [4]
- e) List out the steps in FPGA design flow. [3]
- f) Write about configuration modes. [4]

PART-B (3x16 = 48 Marks)

2. a) Explain the structures of n MOS enhancement mode, depletion mode and p-MOS enhancement mode transistors. [8]
- b) Draw and explain the operation of BiCMOS inverter. [8]
3. a) What is a stick diagram and explain about different symbols used for components in stick diagram. [8]
- b) Design a stick diagram and layout for the CMOS logic shown below.
 $Y = \overline{(AB)} + \overline{(CD)}$ [8]
4. a) Realize basic gates using NMOS. [8]
- b) Explain scaling factors for device parameters. [8]
5. a) Explain the structured design approach of parity generator. [8]
- b) Explain the design of a 4-bit shifter. [8]
6. a) Explain the stuck at fault model with example. [8]
- b) Explain about the clocking mechanism. [8]
7. a) Explain the FPGA design process. [8]
- b) Explain the concept of sheet resistance. [8]