

Code No: **RT41046****R13****Set No. 1****IV B.Tech I Semester Supplementary Examinations, February/March - 2018****ANALOG IC DESIGN****(Electronics and Communication Engineering)****Time: 3 hours****Max. Marks: 70***Question paper consists of Part-A and Part-B**Answer ALL sub questions from Part-A**Answer any THREE questions from Part-B*

\*\*\*\*\*

**PART-A (22 Marks)**

1. a) Define sheet resistance. [4]
- b) Define sensitivity of a voltage reference. [4]
- c) Classify output amplifiers. [4]
- d) Define slewrate and derive an expression for it. [4]
- e) What is autozeroing technique? [3]
- f) Explain how skew reduction is done using PLL. [3]

**PART-B (3x16 = 48 Marks)**

2. a) Discuss about various capacitances in a MOSFET and derive relation between them. [8]
- b) Derive the sub threshold MOS model and explain about it. [8]
3. a) Draw and analyze cascode current mirror. [8]
- b) Explain about the effect of temperature of voltage references. [8]
4. a) Explain the operation of active load inverter. [8]
- b) Using small signal model derive an expression for voltage gain of a differential amplifier. [8]
5. a) Explain the miller compensation in two stage op-amps. [8]
- b) Discuss the operation of folded cascade op-amp. [8]
6. a) What is a comparator? Explain the static and dynamic characteristics of a comparator. [8]
- b) Find the propagation delay of an open loop comparator having a dominant pole at  $10^3 \text{ rad/s}$ , a DC gain of  $10^4$ , a slewrate of  $1 \text{ V}/\mu\text{s}$ , and a binary output swing of  $1 \text{ V}$ . Assume applied voltage is  $10 \text{ mV}$ . [8]
7. a) Discuss about non ideal effects in PLL. [8]
- b) Explain the operation of cross coupled oscillator. [8]