

Code No: RT31026

R13**SET - 1****III B. Tech I Semester Supplementary Examinations, May -2018****LINEAR & DIGITAL IC APPLICATIONS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)2. Answering the question in **Part-A** is compulsory3. Answer any **THREE** Questions from **Part-B****PART -A**

- 1 a) List the advantages of ICs over discrete components? [3M]
- b) Define input offset current and input offset voltage [4M]
- c) Give the important features of an instrumentation amplifier. [4M]
- d) Define capture range and lock range? [4M]
- e) Draw the circuit of first order active filter. [3M]
- f) Compare successive approximation ADC with dual slope ADC. [4M]

PART -B

- 2 a) What is a differential amplifier? Mention the classification of differential amplifier with neat diagrams. [8M]
- b) Explain ac analysis of dual input balanced output differential amplifier configuration. [8M]
- 3 a) What is an operational amplifier? Give its symbol and also draw its electrical equivalent circuit. [8M]
- b) An op-amp has a slew rate of $2\text{V}/\mu\text{s}$. What is the maximum frequency of an output sinusoid of peak value 5V at which the distortion sets in due to the slew rate limitation? [8M]
- 4 a) With a neat sketch explain the instrumentation amplifier [8M]
- b) Draw the circuit of a voltage to current converter if the load is i) floating and ii) Grounded. Are there any limitations as the size of the load when grounded? [8M]
- 5 a) Draw the block diagram of NE/SE565 PLL and explain the operation with the help of waveforms. [8M]
- b) What is meant by VCO? Explain in detail and state the applications of VCO? [8M]
- 6 a) Plot and explain frequency response of [8M]
 - i) Low pass Butter worth filter
 - ii) High pass filter
 - iii) Band pass filter
 - iv) Band Reject filter
- b) Design a second order Low Pass Filter at a high cut off frequency of 2 KHz. Draw the frequency response and the circuit with all components. [8M]
- 7 a) Compare different types of A-D converters [8M]
- b) Find the voltage at all nodes 0, 1, 2 ... and at the output of a 5-bit R-2R ladder DAC. [8M]
The LSB is 1 and all other bits are equal to '0'. Assume $V_R = -10\text{V}$ and $R = 10\text{ k}\Omega$
