

Code No: G6803/R13

M. Tech. I Semester Supplementary Examinations, Jan/Feb-2018

**CMOS ANALOG IC DESIGN****(Common to VLSI & ES, ES & VLSI, VLSID & ES, ES & VLSID, VLSI, VLSID, VLSID, VLSI&ME)****Time: 3 hours****Max. Marks: 60**

---

*Answer any FIVE Questions*  
*All Questions Carry Equal Marks*

---

- |      |  |     |
|------|--|-----|
| 1. a | Explain about the CMOS device Modeling   | 6M  |
| b    | Explain about the computer simulation models   | 6M  |
| 2.   | What is Current Mirror .Explain the general properties of current mirrors with block diagram | 12M |
| 3. a | Explain the difference between cascade current mirror and Wilson current mirror              | 6M  |
| b    | Write a short notes on current sinks and sources   | 6M  |
| 4. a | Explain about the design of CMOS opamps  | 6M  |
| b    | Derive the expression for power-supply rejection ratio of Two-stage op-amps                  | 6M  |
| 5. a | Differentiate the Two-stage comparator and Discrete time Comparator                          | 6M  |
| b    | Explain about the different types of Open loop comparator                                    | 6M  |
| 6. a | Explain about the design of Two-stage op-amps  | 6M  |
| b    | Explain about the Cascode Op-amps  | 6M  |
| 7. a | Explain about the Delay Locked Loops   | 6M  |
| b    | Discuss about the Oscillator applications  | 6M  |
| 8. a | Define Oscillator. Explain about the Ring Oscillator with an example                         | 6M  |
| b    | Discuss various types of open loop comparators   | 6M  |

\*\*\*\*\*