

Code No : I6801/R16

M. Tech. I Semester Regular/Supple Examinations, Jan/Feb-2018

DIGITAL SYSTEM DESIGN

(Common to VLSI&ES, ES&VLSI, VLSID&ES, ES&VLSID, VLSI, VLSID, VLSISD, VLSI&ME, ES, DE&CE, DE&CS, E&CE, C&CE, C&C and I&CS)

Time: 3 hours

Max. Marks: 60

Answer any FIVE Questions
All Questions Carry Equal Marks

1. Minimize the following switching function using CAMP Algorithm.
 $f(a, b, c, d) = \sum m(1, 3, 5, 7, 9, 10, 13, 14, 15)$ 12M
2. Determine the Essential Prime Cubes for the following four variable single output function using IISc Algorithm.
 $f = 0200 + 1102 + 2201 + 0011 + 0010$ 12M
3. Find a simple column PLA folding of the following SSR Table and draw the folded PLA. 12M

Columns	SSR
A	14
B	1, 3
C	3, 4, 5, 9, 12
D	1, 2, 5, 10, 11, 15
E	2, 4, 7, 8, 10, 15, 16
F	1, 2, 15
G	6, 8, 11, 13
H	3, 5, 6, 14, 15
I	7, 10, 12, 13, 16
J	4, 9, 16

4. Determine the minimal test set to detect various faults for a given PLA which is having four inputs (x_1, x_2, x_3 and x_4), two outputs (z_1 and z_2) and five product terms (p_1, p_2, p_3, p_4 and p_5). The functions realized are 12M

$$Z_1 = p_1 + p_2 + p_3$$

$$Z_1 = x_1^1 x_3^1 + x_3^1 x_4 + x_1 x_3$$

$$Z_2 = p_2 + p_4 + p_5$$


$$Z_2 = x_3^1 x_4 + x_2 x_3 x_4^1 + x_1 x_2 x_3$$
5. Determine the distinguishing sequence for the following machine M by conducting adaptive distinguishing experiment. 12M

Code No : I6801/R16

PS	Machine M	
	NS, Z	
	X = 0	X = 1
A	D, 0	C, 0
B	C, 1	D, 1
C	B, 1	A, 0
D	A, 0	A, 0

6. A Two Level AND – OR logic circuit has two AND gates feeding one OR gate. The two AND gates realize the product terms $x_1 x_2^1$, $x_2 x_3$ respectively. Derive the a and b tests for detecting SA1 fault on the line x_2^1 . Find a minimum test set for the network shown.

12M

 

7. Design a digital system with two Flip-flops E and F and one 4 bit binary counter A. The individual flip flops in A are denoted by A_4 , A_3 , A_2 and A_1 with A_4 holding the most significant bit of the count. A start signal S initiates the system operation by clearing the counter A and flip flop F. The counter is then incremented by one starting from the next clock pulse and continues to increment until operations stop. Counter bits A_3 and A_4 determine the sequence of operations: if $A_3=0$, E is cleared to Zero and the Count Continues. If $A_3=1$, E is set to 1; then if $A_4=0$, the count continues, but if $A_4=1$, F is set to one on the next clock pulse and the system stops counting.

12M

8. Write notes on any Two of the following.
- ROM Design
 - Kohavi Algorithm
 - DFT schemes

12M
