

**Code No: MC1312/R13****MCA I Semester Supplementary Examinations, January-2018****DIGITAL LOGIC AND COMPUTER ORGANIZATION****Time: 3 Hours****Max. Marks: 60**

---

*Answer Any FIVE Questions  
All Questions Carry Equal Marks*

---

- |      |   |     |
|------|---|-----|
| 1. a | Convert the following binary number to their equivalent decimal and hexadecimal (base 16) representation. i) 101101.0101 ii) 1010.0111 iii) 10.01 | 6M  |
| b    | Discuss the Logic Gates with neat sketches.   | 6M  |
| 2. a | Explain DTL and TTL NAND Gates.   | 6M  |
| b    | Realize the expression $g = a.b.c' + d + f' + a.e'$ using NAND gates.   | 6M  |
| 3. a | Perform the following arithmetic operations assuming that the decimal digits are coded in 8421 code<br>i) 24+16 ii) 12+13 iii) 84 - 97            | 6M  |
| b    | Explain a Four-bit Adder with neat sketch.  | 6M  |
| 4. a | Define addressing mode? Explain direct addressing mode with example.  | 6M  |
| b    | Write the features of SMAC2.  | 6M  |
| 5. a | Define ROM? Explain it.   | 6M  |
| b    | What is Interrupt? Explain Single level Interrupt Processing.   | 6M  |
| 6.   | Draw the functional block diagram of Dynamic Random Access Memory and explain it.   | 12M |
| 7. a | Define Control Memory? Explain Micro program Sequencer.   | 6M  |
| b    | Write a note on register sets.  | 6M  |
| 8.   | Design the combinatorial circuits with multiplexers.  | 12M |

\*\*\*\*\*