

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech.(EE)/(Electrical & Electronics)/(Electronics & Electrical)(2011 onwards)
B.Tech.(Electrical Engineering & Industrial Control) (2012 Onwards)
(Sem.-4)

DIGITAL ELECTRONICS

Subject Code : BTEC-404

Paper ID : [A1207]

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTION TO CANDIDATES :

1. **SECTION-A is COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. **SECTION-B** contains **FIVE** questions carrying **FIVE** marks each and students has to attempt any **FOUR** questions.
3. **SECTION-C** contains **THREE** questions carrying **TEN** marks each and students has to attempt any **TWO** questions.

SECTION-A

1. **Answer briefly :**
 - a. What is Hamming code? Discuss.
 - b. What do you mean by BCD code? Explain.
 - c. Differentiate between multiplexer and an encoder.
 - d. State DeMorgan's theorems.
 - e. What is the significance of Truth table? Discuss.
 - f. Differentiate between RAM and ROM.
 - g. What do you mean by VHDL? Discuss.
 - h. Discuss the significance of T flip-flop.
 - i. Explain the terms Fan-in, Fan-out and unit load with respect to the logic families.
 - j. What are the advantages of R-2R ladder digital to analog converter over weighted resistor type digital to analog converter?

SECTION-B

2. Discuss Binary, Octal and Hexadecimal number systems. Convert the binary number 101010101 to hexadecimal and octal numbers.
3. **Reduce** the following expression to simplest **Sum of product** from using K-Map

$$\Sigma m(0,1,2,10,11,12,13)$$

4. Draw the logic diagram and explain the working of JK flip-flops.
5. Discuss TTL and RTL logic families.
6. Explain the programmable logic arrays in detail.

SECTION-C

7. Draw and explain the working of a successive approximation and dual slope type A/D converters.
8. Discuss the following :
 - a. Decision control structure using VHDL.
 - b. Direct coupled transistor logic.
9. Draw and explain the working of :
 - a. 4-bit up counter.
 - b. Half and Full Adder.