

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech.(Electronics & Computer Engg.) (2011 Onwards) (Sem.-6)

DIGITAL SYSTEM DESIGN

Subject Code : BTEL-606

Paper ID : [A2345]

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTION TO CANDIDATES :

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.
3. SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.

SECTION-A**Q.1 Answer briefly :**

- a) Differentiate between combinational and sequential circuits with example.
- b) Define state table and state assignment.
- c) What do you understand by positive logic and negative logic?
- d) Enlist all logical operators.
- e) What do you understand by essential hazards?
- f) Find complement of $AB' + BC' + C'D$
- g) Enlist various types of ROMs.
- h) What is significance of Data Flow Diagram?
- i) Differentiate between ROM and PLA.
- j) What is the importance of unused states in design of synchronous circuits?

SECTION-B

Q.2 Define and discuss with suitable examples, all types of overloading in VHDL.

Q.3 Specify the method that is used to construct a state table.

Q.4 Write a short note on FPGA.

Q.5 Write a VHDL code for 4:1 multiplexer using behavioral modeling.

Q.6 What do you mean by operators? Explain all six different types of operators.

SECTION-C

Q.7 What are the data objects? Explain briefly all data types.

Q.8 Design a counter which counts the following sequence :

0,8,12,14,19,13,11,15,0,8,12.....

Use clocked J-K FF and NAND gates.

Q.9 Draw the functional partition of PoP vending machine control system. Explain briefly.