

Roll No.

--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 03

Total No. of Questions : 08

M.Tech. (VLSI D) (2016 & Onwards) (Sem.-2)

TESTING AND FAULT TOLERANCE

Subject Code : MTVL-202

Paper ID : [74259]

Time : 3 Hrs.

Max. Marks : 100

INSTRUCTIONS TO CANDIDATES :

1. Attempt any FIVE questions out of EIGHT questions.
2. Each question carries TWENTY marks.

Q1 Explain the following faults :

- | | |
|--------------------|----------------------|
| a) Stuck-Open | c) Stuck-Short fault |
| b) Transient fault | d) Untestable fault |
- (4×5=20)**

Q2 Explain fault dominance and checkpoint theorem. For the circuit as shown in Figure I: **(20)**

- a) What is the number of all potential fault sites?
- b) Derive the equivalence collapsed set. What is the collapse ratio?
- c) Derive the dominance collapsed set. What is the collapse ratio?

 


Figure 1 : Circuit diagram for problem 2.

- Q3 a) Explain even-driven simulation with the help of suitable example. (10)
- b) Assuming a four-bit machine word, demonstrate parallel fault simulation of vector (1,0,1) for the three single stuck-at-1 faults on the second primary input and its two fanouts, respectively, in the circuit of Figure 2. (10)

 


Figure 2 : Circuit for problem 3.

- Q4 a) Explain different SCOAP controllability and observability metrics for combination circuits. (10)
- b) Compute the SCOAP controllability and observability metrics for circuit given in Figure 3. (10)

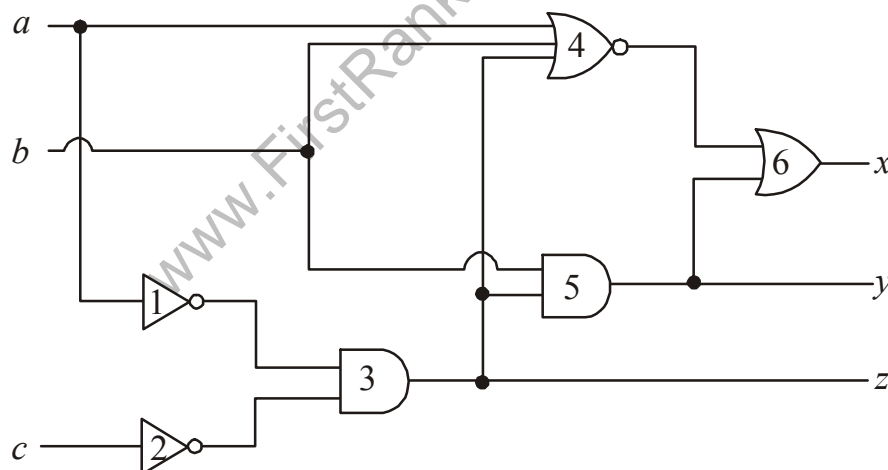


Figure 3 : Circuit for Problem 4.

- Q5 a) Discuss path sensitization method of test pattern generation. (10)

- b) Use Roth's D-ALG to perform ATPG for the sa 1 and for the sa 0 fault on the fanout branch h in the circuit shown in Figure 4 (10)

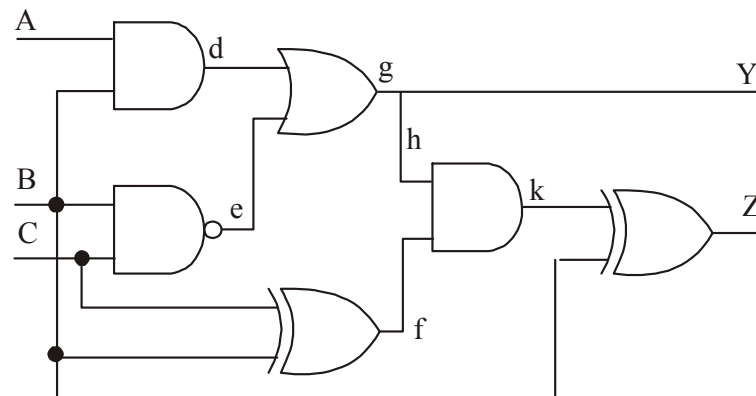


Figure 4: Circuit for Problem 5.

- Q6 a) How do you perform generic boundary scan? (10)
- b) Given two LFSR of polynomial $X^4 + X^3 + 1$ and $X^4 + X^2 + 1$ determine the m-sequence generated by LSB FFs with seed value '1000' and also compute the cycle length (LC) for both the LFSR.
- Q7 a) Explain about TAP controller used in test-bus circuitry (10)
- b) Draw the block diagram for a BIST implementation using BIBO and explain the test procedure. (10)
- Q8 Write short notes on : (4×5=20)
- a) Boundary scan standards
 - b) Error collection codes
 - c) Reconfiguration techniques
 - d) Yield modeling reliability