

R09

Code: 9A02304

B.Tech II Year I Semester (R09) Supplementary Examinations, May 2013

BASIC ELECTRICAL & ELECTRONICS ENGINEERING

(Biotechnology)

Time: 3 hours

Max. Marks: 70

All questions carry equal marks

A total of five questions are to be answered with at least two questions from each part

Use separate booklets for Part A and Part B

PART - A

- 1 (a) State and explain Kirchoff's laws.
(b) Explain any one passive element in detail.
- 2 (a) Define and derive the expression for average value of a sinusoidal voltage wave form.
(b) Show that power dissipated by a pure inductive circuit excited by a sinusoidal voltage source is zero.
- 3 Derive the relation between phase and line values of a 3-phase balanced delta connected system with neat phasor diagram and also derive the expression for power in a 3- ϕ balanced delta connected systems.
- 4 (a) Explain the characteristics of DC generators.
(b) Explain the principle of operation of 3-phase induction motors.

PART - B

- 5 (a) What is a PN junction diode? Draw and explain the $v - i$ characteristics of a junction diode when it is as forward biased and reverse biased.
(b) Draw and explain the principle of operation of half wave rectifier.
- 6 (a) Explain the input and output characteristics of a transistor in CE configuration.
(b) What are the necessary conditions for an oscillator to give sustained oscillations?
- 7 (a) Explain the basic principle of operation of dielectric heating.
(b) What is welding? What is meant by resistance welding?
- 8 (a) Explain the principle of operation of cathode ray tube.
(b) Derive the expression for electrostatic deflection sensitivity of CRT.
