

Code: 9A04402

1

B.Tech II Year II Semester (R09) Regular & Supplementary Examinations, April/May 2013

ELECTRONIC CIRCUIT ANALYSIS

(Common to EIE, E, Con.E and ECE)

Time: 3 hours

Max Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 (a) What are the different types of distribution in amplifier? Explain each.
(b) By using Hybrid model derive performance characteristics for CB transistor amplifier.
- 2 Draw the circuit diagram of two stage RC-coupled transistor amplifier. Explain operation and calculate the mid and low frequency ranges.
- 3 (a) What is miller's theory? Derive millers' output capacitance using millers' effect capacitance.
(b) The input power to a device is 10000 W at a voltage of 1000 V. The output power is 500 W and output impedance is 20 Ω .
 - (i) Find the power gain in decibels.
 - (ii) Find the voltage gain in decibels.
- 4 (a) Explain the terms "impedance matching" and "cross-over distortion".
(b) Explain why the complimentary symmetry power amplifier has become more popular in modern circuits.
- 5 (a) Draw the equivalent circuit of a capacitance coupled single tuned amplifier and derive the equation for voltage gain.
(b) Calculate the maximum bandwidth of a cascaded single-tuned amplifier with a gain of 43.4 dB, given $g_m = 2 \text{ m A/v}$ and $C = 300 \text{ pF}$.
- 6 Explain the principle of stagger tuning technique of transformer-coupled amplifier that is used to obtain band pass characteristic with pass band of 10 KHz.
- 7 With reference to voltage regulators discuss about:
 - (a) Output resistance.
 - (b) Load regulation.
 - (c) Line regulation.
 - (d) Stability factor.
 - (e) Temperature co-efficient.
 - (f) Ripple regulation.
- 8 (a) List out the important features of 3-terminal regulators.
(b) What are the limitations of linear regulators over switched mode power supplies?

Code: 9A04402

2

B.Tech II Year II Semester (R09) Regular & Supplementary Examinations, April/May 2013

ELECTRONIC CIRCUIT ANALYSIS

(Common to EIE, E, Con.E and ECE)

Time: 3 hours

Max Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 (a) Draw the circuit of an emitter follower and its equivalent circuit. List out its characteristics.
(b) The h-parameters of the transistor used in CE amplifier are $h_{fe} = 50$, $h_{ie} = 1.1 \text{ K}$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 24 \mu\text{A/V}$. Find out current gain and voltage gain with and without source resistance, input and output impedances, given that $R_L = 10 \text{ K}$ and $R_S = 1 \text{ K}$.
- 2 Draw the circuit diagram of two stages RC coupled transistor amplifier. Explain operation. Calculate the mid frequency range and low frequency range.
- 3 (a) Derive the expression for CE short circuit current gain and explain the hybrid π model.
(b) The low frequency parameters of a transistor are given below. $V_{cc} = 5 \text{ V}$, $I_c = 10 \text{ MA}$, $h_{ie} = 500 \Omega$, $h_{oe} = 4 \times 10^5 \text{ A/V}$, $h_{fe} = 10^4$, $f_p = 50 \text{ MHz}$, $C_{ob} = 3 \text{ pf}$. Compute the values of all hybrid π parameters.
- 4 (a) What are the two disadvantages of push pull amplifier?
(b) Give the schematic of class B push pull amplifier with complimentary symmetry and explain its working.
- 5 (a) State the functions and frequency range of operations of tuned amplifiers with relevant reasons.
(b) Draw the circuit of typical single tuned RF amplifier stage employing a transistor. Explain its operation. If the tuned circuit contains $L = 200 \text{ micro Henry}$, $S_C = 120 \text{ pF}$ and $R_L = 5 \text{ k}\Omega$, calculate its bandwidth.
- 6 Draw the circuit of a class C – tuned amplifier and explain its operation. Derive the efficiency of the amplifier is 100% making necessary assumption.
- 7 (a) Explain the need for voltage regulation?
(b) What is meant by voltage multiplier? List out the names of 4 different multipliers. Explain their working.
- 8 (a) What are the limitations of 3-terminal regulators?
(b) Design an adjustable voltage source using LM 317 for the following specifications :
 $V_0 = 9 \text{ and } 15 \text{ v}$; $I_0 = 1 \text{ A}$.

Code: 9A04402

3

B.Tech II Year II Semester (R09) Regular & Supplementary Examinations, April/May 2013

ELECTRONIC CIRCUIT ANALYSIS

(Common to EIE, E, Con.E and ECE)

Time: 3 hours

Max Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 (a) Draw the small signal model of CE amplifier and derive the expression for its A_i , A_v , R_i and R_o .
(b) For the emitter follower with $R_S = 500 \Omega$ and $R_L = 5 \text{ k}\Omega$, Calculate A_i , A_v , A_{vS} and R_o . Assume $h_{fe} = 50$, $h_{ie} = 1 \text{ k}\Omega$, $h_{oe} = 25 \text{ mA/V}$.
- 2 (a) Describe the operation of transformer coupled amplifier and also derive the expression for its current gain.
(b) With relevant circuit explain the different coupling schemes used in amplifiers.
- 3 (a) Describe the emitter follower at high frequency and also derive the equation for higher cutoff frequency.
(b) With hybrid π equivalent circuit, derive the expressions for hybrid conductances.
- 4 (a) Distinguish between cross-over distortion and harmonic distortion. How they can be eliminated?
(b) Determine the component values of class A series feed amplifier to deliver 75 mW of output power to a load of 4 ohm $V_{CC} = 16 \text{ V}$. At the operating point $I_B = 200 \text{ micro Amp}$, $P_o(\text{max}) = 200 \text{ mW}$.
- 5 (a) Draw the circuit of double-tuned transformer coupled amplifier. Discuss the nature of the response of the amplifier for different values $kQ = 1$; $kQ > 1$ and $kQ < 1$.
(b) How many stages are required to obtain gain of $A = 100$ using a tuned amplifier with BW of 500 KHz at $f_o = 10 \text{ MHz}$. $C = 100 \text{ pF}$ and $g_m = 2 \text{ mA/V}$.
- 6 (a) Explain the method of adjusting the amplifiers for stabilization of the response.
(b) Explain the low frequency compensation technique to increase the BW of an amplifier.
- 7 (a) List out different types of voltage regulators. What are the advantages and disadvantages of each type?
(b) A certain voltage doubler has 20 V rms at its input. What is the output voltage? Sketch the circuit indicating the input terminals and PIV rating of the diode.
- 8 (a) Draw the circuit diagram of a 3-terminal regulator as a current source and explain its operation.
(b) Design a voltage regulator using 723 to give an output voltage of 5 V at 0.1 A current. $V_i = 10 \text{ V}$ and $V_{SC} = 0.65 \text{ V}$.

Code: 9A04402

4

B.Tech II Year II Semester (R09) Regular & Supplementary Examinations, April/May 2013

ELECTRONIC CIRCUIT ANALYSIS

(Common to EIE, E, Con.E and ECE)

Time: 3 hours

Max Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 (a) Draw the small signal hybrid model of CB amplifier and derive an expression for its A_V , A_i , R_i and R_o .
(b) The h-parameters of CE amplifier are $h_{ie} = 1100 \Omega$, $h_{fe} = 50$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 24 \mu A/V$ and $R_S = 1 k\Omega$, $R_L = 10 k\Omega$. Find the current and voltage gain, (with and without source resistance) input & output impedances.
- 2 (a) Compare emitter follower and Darlington emitter follower configurations in respect of:
(i) Current gain. (ii) Input impedance. (iii) Voltage gain. (iv) Output impedance.
(b) If four identical amplifiers are cascaded each having $f_L = 100$ Hz, determine the overall lower 3 dB frequency. Assume non-interacting stages.
(c) Write a short note on Gain-Band width product of amplifiers.
- 3 (a) Derive all components in the hybrid π model in terms of h parameters in CE configuration.
(b) Describe the emitter follower at high frequency and also derive the equation for higher cutoff frequency.
- 4 (a) Compare series fed and transformer coupled class A power amplifiers.
(b) Draw the circuit of transformer coupled amplifier and explain the operation graphically.
- 5 (a) Draw a simple BJT tuned amplifier circuit and its ideal response characteristic.
(b) Calculate the resonant frequency, BW and Q of the tuned transformer amplifier with $R_L = 10 k\Omega$, $C = 30$ pF and $L = 10$ mH and turns ratio = 10.
- 6 (a) What are the main advantages of class-C RF amplifier and explain its operation with necessary waveforms?
(b) Mention the 3-methods of stabilization of double-tuned transformer coupled amplifier circuit performance against the feedback path through the parasitic capacity between input and output and also mention reasons for neutralization schemes.
- 7 (a) Explain the limitations of unregulated power supplies. To derive regulated DC output from AC mains, what are the important building blocks required. Explain about each block.
(b) A certain voltage doubler has 20 V rms at its input. What is the output voltage? Sketch the circuit indicating the input terminals and PIV rating of the diode for (i) Voltage Tripler and (ii) Quadrupler.
- 8 (a) Draw the circuit of 7805 voltage regulator and explain its operations.
(b) 7824 regulator IC can deliver a maximum current of 700 mA. Design a circuit using 7824 to deliver a current of 3 A.
