

Code No: R21042

**R10****SET - 1****II B. Tech I Semester, Regular Examinations, Nov – 2012****NETWORK ANALYSIS**


(Com. to ECE, EIE, ECC)

Time: 3 hours


Max. Marks: 75

Answer any **FIVE** Questions  
All Questions carry **Equal** Marks

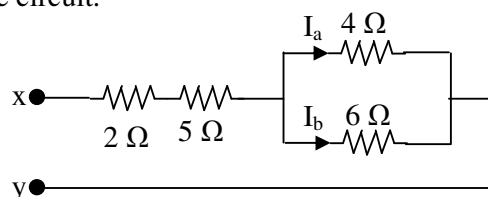1. a) What are the types of sources? Explain them with suitable diagrams and characteristics?  
b) Calculate the voltage that is to be connected across terminals x-y is shown in below figure such that the voltage across the  $2\Omega$  resistor is 10 V. Also find  $I_a$  and  $I_b$ . what is the total power loss in the circuit.



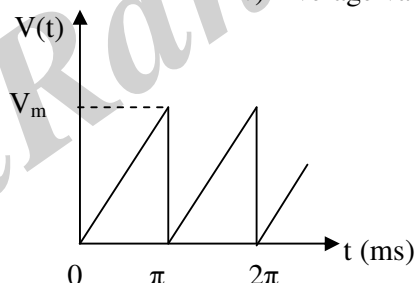2. Explain the principles of duality? Write a graphical procedure to draw a dual network?  
A periodic voltage waveform has been shown in the below figure. Determine the following.  
i) Frequency of the waveform      ii) Wave equation for  $0 < t < 100$  m sec  
iii) R.M.S. value and                  iv) Average value




3. a) Define the following  
i) Impedance      ii) Phase angle      iii) Power factor  
b) State and explain star-delta conversion in AC systems.


Code No: R21042

**R10****SET - 1**

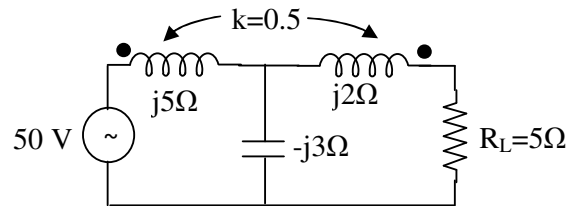
4. For the network shown in below figure, find the voltage across load resistance  $R_L$ .



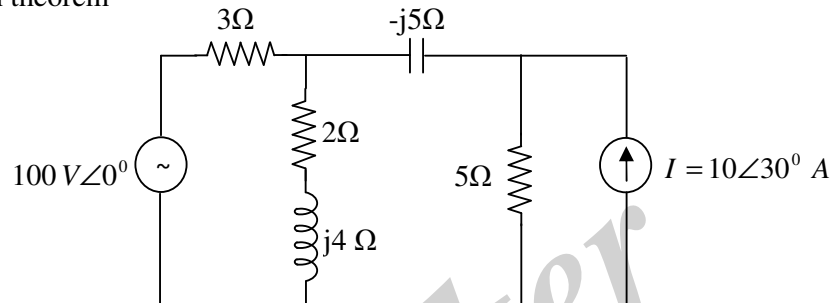
5. Find the current through the capacitor of  $-j5\Omega$  reactance as shown in below figure using superposition theorem



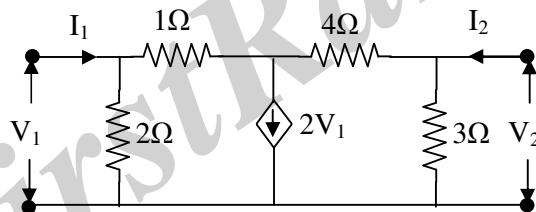6. Find the open circuit impedance parameters of the circuit shown in below figure. Also find the Y-parameters



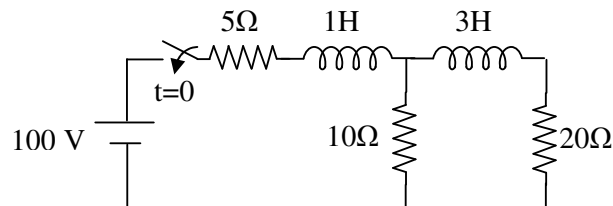7. In the network shown in below figure, the switch is closed at  $t=0$ . Find the value of current in each loop.



8. a) What are the properties of filters  
 b) Design an m-derived T-section low pass filter having cut off frequency,  $f_c=7000\text{Hz}$ , design impedance  $R_o=600\Omega$  and frequency of infinite attenuation.

Code No: R21042

**R10****SET - 2****II B. Tech I Semester, Regular Examinations, Nov – 2012****NETWORK ANALYSIS**


(Com. to ECE, EIE, ECC)

Time: 3 hours

Max. Marks: 75

Answer any **FIVE** Questions  
All Questions carry **Equal** Marks

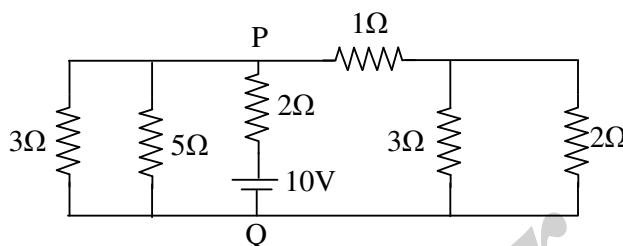1. a) What are the network elements? Explain them  
b) What is the magnitude of current drained from the 10V source in the circuit shown below?



2. a) Define the following terms  
i) Node                      ii) Tree                      iii) Incidence matrix                      iv) Basic tie set  
b) A non-alternating periodic waveform has been shown in below figure. Find its form factor and peak factor




3. a) Obtain the expressions for star-delta equivalence of impedance network.  
b) A two element series circuit is connected across AC source  $e(t) = 200\sqrt{2} \sin(\omega t + 20^\circ) V$ . The current in the circuit then found to be  $i(t) = 10\sqrt{2} \cos(\omega t - 25^\circ) A$ . Determine the parameters of the circuit.
4. a) Derive the expression for bandwidth of series RLC circuit.  
b) Two coils with 300 turns and 700 turns are wound side by side on a closed magnetic circuit of area of cross section  $400\text{cm}^2$  and mean length 80 cm, the magnetic circuit has relative permeability of 4000. Determine the mutual inductance, self induced e.m.f and mutually induced e.m.f when the current in the coil with 300 turns grows from zero to 25A in a time of 0.3 sec


Code No: R21042

**R10****SET - 2**

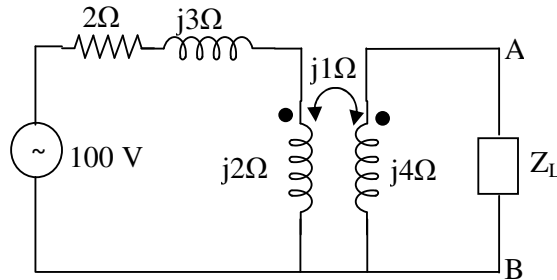
5. Obtain equivalent circuit across A-B terminals in figure shown below and find the value of  $Z_L$  to have maximum power.



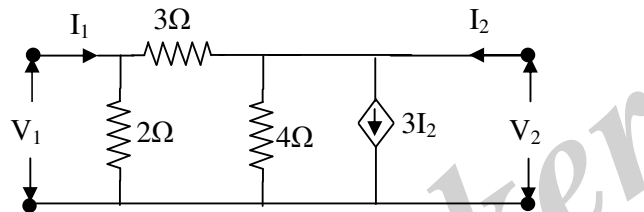6. Determine Y-parameters of the network shown in below figure



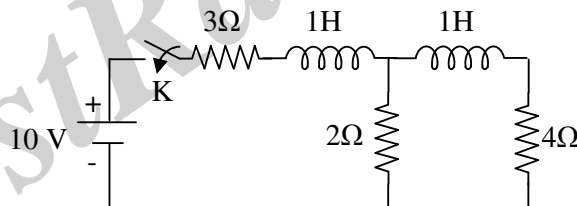7. Using Laplace transformation technique, find current in each loop at  $t = 0^+$  following switching at  $t = 0$  of switch K is shown in below figure. Assume the network previously de-energized.



8. a) What are the classifications of filters? Discuss them briefly.  
 b) Design a constant k-low pass filter having  $f_c = 2$  kHz and design impedance  $R_o = 600\Omega$ . Obtain the value of attenuation at 4 kHz.

Code No: R21042

**R10****SET - 3****II B. Tech I Semester, Regular Examinations, Nov – 2012****NETWORK ANALYSIS**


(Com. to ECE, EIE, ECC)

Time: 3 hours


Max. Marks: 75

Answer any **FIVE** Questions  
All Questions carry **Equal** Marks

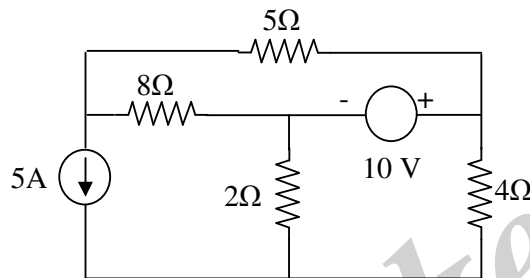
1. a) Explain the source transformation techniques with suitable circuits.  
b) Find mesh currents and determine voltage across each element in the circuit shown in below Figure.



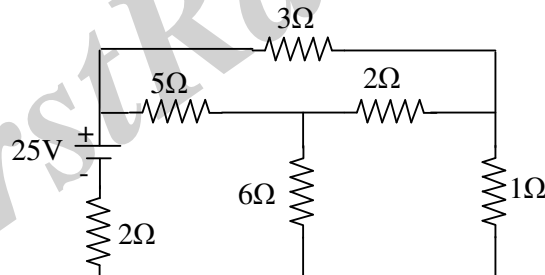2. a) Explain the RMS value and average value of alternating quantity. Derive its necessary expressions.  
b) Find the branch currents shown in below figure by using the concept of the tie-set matrix.



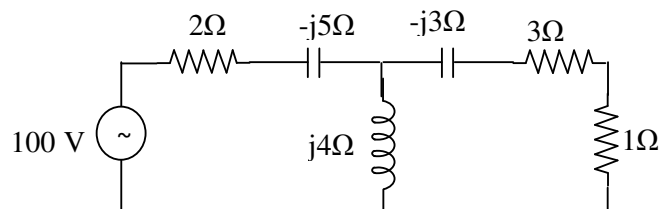
3. In the two-mesh network shown in below figure, determine the  
a) Mesh currents  
b) Power supplied by the source and  
c) Power dissipated in each resistor




Code No: R21042

**R10****SET - 3**

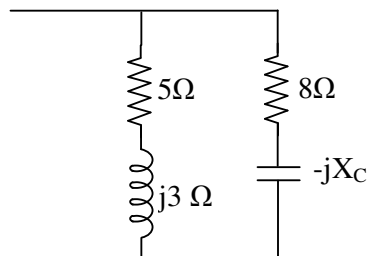
4. a) Determine the coefficient of coupling of two magnetically coupled coils of turns  $N_1$  and  $N_2$   
 b) For the circuit shown in below figure, find the value of  $X_c$  in ohms at which the circuit under resonance



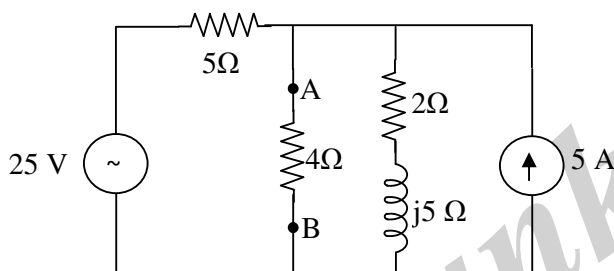
5. In the circuit shown in below figure, find the current through  $R_L$  connected across A-B terminals by utilizing Thevenin's theorem. Verify the results by Norton's theorem.



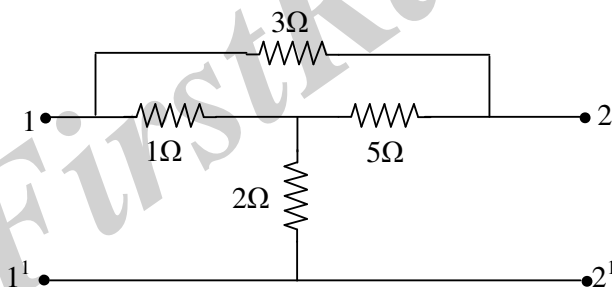6. For the network shown in below figure, find ABCD parameters



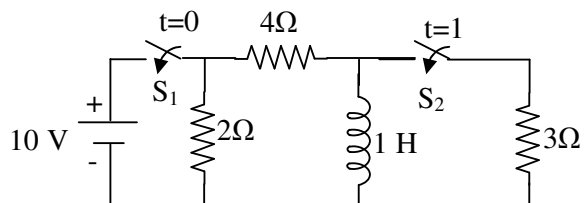7. In the network shown in below figure find the current through the inductor for all values of 't'.



8. a) Explain the concept of m-derived filters.  
 b) Design a prototype band stop filter section having cut-off frequencies of 2000 Hz and 5000 Hz and design resistance of  $600\Omega$ .

Code No: R21042

**R10****SET - 4**

**II B. Tech I Semester, Regular Examinations, Nov – 2012**  
**NETWORK ANALYSIS**  
 (Com. to ECE, EIE, ECC)


Time: 3 hours

Max. Marks: 75


Answer any **FIVE** Questions  
 All Questions carry **Equal** Marks

~~~~~

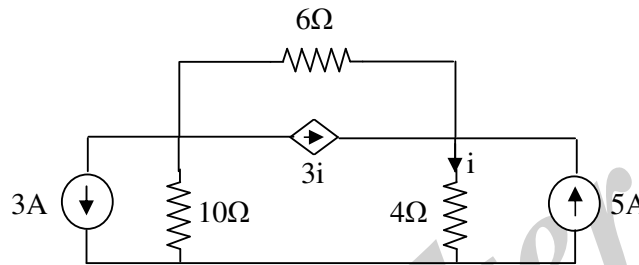
1. a) State and explain Kirchoff's laws.  
 b) Using nodal analysis techniques to determine current 'i' in the network shown in below figure.



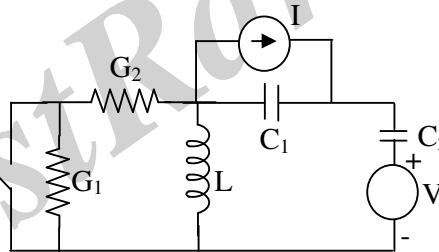2. a) Define the following  
 i) Time period      ii) Frequency      iii) RMS value      iv) Average value  
 b) Draw the dual of the network shown in below figure and explain its procedure.



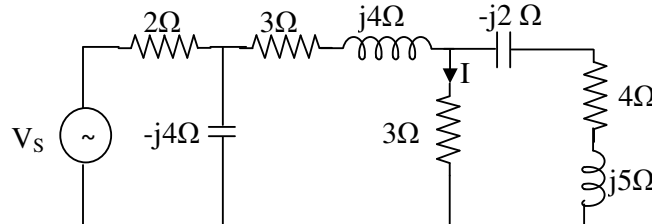3. Find the source voltage 'V<sub>s</sub>' by using nodal technique, assume  $I = 5 \angle 45^\circ$  A.




4. a) Contrast between magnetic circuits and electrical circuits.  
 b) A series RLC circuit has the following parameters.  $R = 15$  ohms,  $L = 2$ H,  $C = 100$  micro F. Calculate the resonant frequency. Under resonant condition, calculate current, power, and voltage drops across various elements, if the applied voltage is 100V.


Code No: R21042

**R10****SET - 4**

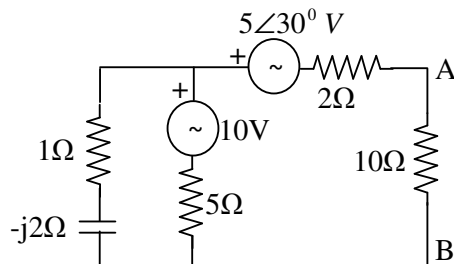
5. Find the current through the 10 ohm resistor in the following circuit using Norton's Theorem.



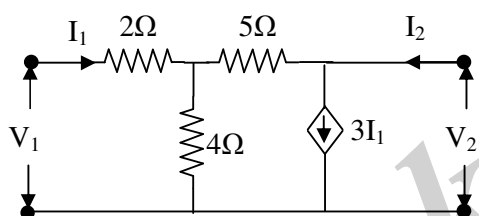6. Obtain Z-parameters and transmission parameters of the network shown in below figure.



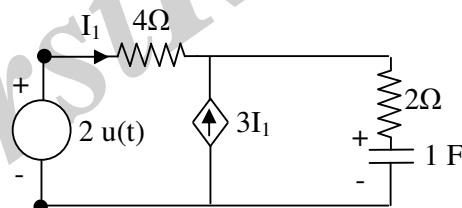7. In the below figure, the initial voltage in the capacitor is 1V as the polarity shown. Find the voltage appearing across the capacitor with application of the step voltage



8. a) Explain the analysis of band pass filter.  
b) Design a T-section constant K-high pass filter having cut-off frequency of 10 kHz and design impedance  $R_0 = 600$  ohms. Find its characteristic impedance and phase constant at 25 kHz.