

Code No: A5505

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

M.Tech. I Semester Examinations, April 2011

ANALOG & DIGITAL IC DESIGN

(EMBEDDED SYSTEMS)

Time: 3 hours

Max. Marks.60

Answer any Five Questions
All questions carry equal marks

- - -

1. a) Explain in detail different types of noise in OPAMPS.
b) Derive the equation for the upper limit on the unity gain frequency of a cascade gain stage amplifier. [12]
2. a) Derive the equation for the transfer function of a common source amplifier in the high frequency analysis.
b) Explain about noise bandwidth in OPAMPS. [12]
3. a) Explain working of Basic Charge-Pump PLL with neat diagrams.
b) Derive the equation for frequency of oscillation in a switched-capacitor relaxation oscillator. [12]
4. a) What is a signal Flow Graph? Draw and explain the signal flow graph of a three input switched capacitor integrator.
b) Explain the two methods for realizing the peak detectors. [12]
5. a) Write the structural model VHDL code for an 8-bit counter using D-Flip Flop as component.
b) Compare the logic families with respect to speed, propagation delay, Noise margin, Fan in, Fan out and power dissipation. [12]
6. a) Explain all the advanced features of the Xilinx 4000 Series FPGAS.
b) Explain in detail about the internal structure of ROM with neat diagrams. [12]
7. a) Explain about the R-2R based converters with necessary equations and diagrams.
b) Explain Successive Approximation A/D converter with a neat circuit diagram. [12]
8. Write short notes on any **TWO**
 - a) Wilson wider current mirror
 - b) Voltage controlled Oscillator
 - c) Barrel shifter [12]
