

**NR/R09**

**Code No: B4301 / D4301, D5401**

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**

**M.Tech II Semester Examinations, March/April 2011**

**POWER ELECTRONIC CONTROL OF AC DRIVES**

**(COMMON TO POWER ELECTRONICS, POWER ELECTRONICS & ELECTRIC DRIVES)**

**Time: 3hours**

**Max.Marks:60**

**Answer any five questions  
All questions carry equal marks**

---

1. a) Explain torque production in an induction motor.  
b) Explain induction motor characteristics in constant torque and field weakening regions. [6+6]
2. Explain speed torque characteristics with variable voltage operation, variable frequency operation, constant v/f operation and variable stator current operation. [12]
3. Explain the operation of these phase voltage source inverter fed these induction motor drive with  $180^\circ$  conduction with the help of circuit diagram and waveforms. Also sketch speed-torque characteristics for sub-synchronous speeds? [12]
4. Discuss the working of these phase slip-ring induction motor when static Scheribus scheme is employed for its speed control. Draw a neat circuit, speed-torque characteristics and being out salient features of this drive. [12]
5. What is vector control with respect to induction motor? Explain the operation of induction motor when direct method of vector control is adopted. [12]
6. Discuss different control strategies of synchronous motor with reference to its characteristics. [12]
7. Discuss the working of a three-phase BLDC motor drive when fed from voltage source inverter on closed loop operation. Draw neat circuit diagram. [12]
8. Write short notes on:  
i) Variable reluctance motor drive.  
ii) Static Kramer drive. [12]

\*\*\*\*\*