$\mathbf{R05}$ 

### I B.Tech Examinations,June 2011 ELECTRONIC DEVICES AND CIRCUITS Common to BME, IT, ICE, E.COMP.E, ETM, E.CONT.E, EIE, CSE, ECE, CSSE, EEE

Time: 3 hours

Code No: R05010204

Max Marks: 80

### Answer any FIVE Questions All Questions carry equal marks \*\*\*\*

- 1. (a) Draw the circuit for darlington pair and derive the expressions for  $A_I$ ,  $A_V$ ,  $R_I$  and  $R_0$ .
  - (b) The figure 4b shows a CE amplifier with collector to base bias. Calculate  $A_I$ ,  $A_V$ ,  $R_I$ . The transistor parameters are  $h_{ie}=1.1$ K,  $h_{fe}=50$ ,  $h_{oe}=25\times 10^{-6}$ A/V,  $h_{re}=2.5\times 10^{-4}$ . [8+8]



- 2. (a) Draw the circuit diagram of half wave rectifier with capacitor input filter. Explain the operation with waveforms.
  - (b) A HWR circuit fed a resistive load of 10KΩ through a power transformer having a step-down turns ratio of 8:1 and operated from 230V, 50Hz A.C. Assume the forward resistance of diode to be 40Ω and transformer secondary winding resistance as 12Ω.
    Calculate the maximum, RMS and average values of current, DC O/P voltage and power, efficiency of rectification and ripple factor. [16]
- 3. (a) When an electron is placed in a magnetic field with a period of rotation  $T = \frac{35.5}{B} \times 10^{-12}$  sec. Show that the trajectory of an electron is a circle.
  - (b) What is the radius described by an electron placed in a magnetic field, perpendicular to its motion, when the accelerating potential is 900v, and  $B = 0.01 wb/m^2$ . What is the time period of rotation? [8+8]
- 4. (a) What do you understand by Q point? Explain its significance.
  - (b) For the circuit shown (figure3b), calculate the value of stability factor S to make the circuit thermally stable. Assume  $I_{CO}=1$ nA and  $\theta=4.1 \times 10^{8} \ {}^{0}C/W$ . [8+8]







- 5. (a) Classify various oscillators based on O/P waveforms, circuit components, operating frequencies and feedback used.
  - (b) A phase shift oscillator is to be designed with FET having  $g_m = 5000 \mu s$ , rd=4k $\Omega$  while the resistance in the feedback circuit is 9.7k $\Omega$ . Select the proper value of C and  $R_D$  to have the frequency of oscillations as 5KHZ. [10+6]
- 6. (a) Draw the drain characteristics of depletion type MOSFET. Explain clearly different operating regions in characteristics with proper reasoning.
  - (b) Describe the construction of a light-emitting diode and explain its operational mechanism. [10+6]
- 7. (a) i. What is a zener diode? How does it differ from an ordinary pn-junction rectifier diode?
  - ii. Give the V-I characteristics of zener diode and explain its salient features in relation to that of pn diode.
  - iii. Give the equivalent model of zener diode under the reverse biased condition.
  - (b) Using analytical expression for diode current calculate the dynamic slope resistance of a Ge diode at 290<sup>o</sup>k when forward biased at current of 10  $\mu$ A.

[10+6]

- 8. (a) Define Desensitivity.
  - (b) For large values of D, what is  $A_f$ ? What is the significance of this result?
  - (c) An Amplifier has a mid-frequency gain of 100 and a bandwidth of 200KHz.
    - i. What will be the new bandwidth and gain if 5% negative feedback is introduced?

**R05** 

# Set No. 2

ii. What should be the amount of negative feedback if the bandwidth is to be restricted to 1MHz? [16]

\*\*\*\*

RANKER

**R05** 

### I B.Tech Examinations,June 2011 ELECTRONIC DEVICES AND CIRCUITS Common to BME, IT, ICE, E.COMP.E, ETM, E.CONT.E, EIE, CSE, ECE, CSSE, EEE

Time: 3 hours

Code No: R05010204

Max Marks: 80

[8+8]

### Answer any FIVE Questions All Questions carry equal marks \*\*\*\*

- 1. (a) What do you understand by Q point? Explain its significance.
  - (b) For the circuit shown (figure3b), calculate the value of stability factor S to make the circuit thermally stable. Assume  $I_{CO}=1$ nA and  $\theta=4.1 \times 10^{8} \ ^{\circ}C/W$ .



Figure 3b

- 2. (a) i. What is a zener diode? How does it differ from an ordinary pn-junction rectifier diode?
  - ii. Give the V-I characteristics of zener diode and explain its salient features in relation to that of pn diode.
  - iii. Give the equivalent model of zener diode under the reverse biased condition.
  - (b) Using analytical expression for diode current calculate the dynamic slope resistance of a Ge diode at 290<sup>0</sup>k when forward biased at current of 10  $\mu$ A.

[10+6]

- 3. (a) Define Desensitivity.
  - (b) For large values of D, what is  $A_f$ ? What is the significance of this result?
  - (c) An Amplifier has a mid-frequency gain of 100 and a bandwidth of 200KHz.

 $\mathbf{R05}$ 

# Set No. 4

- i. What will be the new bandwidth and gain if 5% negative feedback is introduced?
- ii. What should be the amount of negative feedback if the bandwidth is to be restricted to 1MHz? [16]
- 4. (a) When an electron is placed in a magnetic field with a period of rotation  $T = \frac{35.5}{B} \times 10^{-12}$  sec. Show that the trajectory of an electron is a circle.
  - (b) What is the radius described by an electron placed in a magnetic field, perpendicular to its motion, when the accelerating potential is 900v, and  $B = 0.01 wb/m^2$ . What is the time period of rotation? [8+8]
- 5. (a) Draw the drain characteristics of depletion type MOSFET. Explain clearly different operating regions in characteristics with proper reasoning.
  - (b) Describe the construction of a light-emitting diode and explain its operational mechanism. [10+6]
- 6. (a) Classify various oscillators based on O/P waveforms, circuit components, operating frequencies and feedback used.
  - (b) A phase shift oscillator is to be designed with FET having  $g_m = 5000 \mu s$ , rd=4k $\Omega$  while the resistance in the feedback circuit is 9.7k $\Omega$ . Select the proper value of C and  $R_D$  to have the frequency of oscillations as 5KHZ. [10+6]
- 7. (a) Draw the circuit diagram of half wave rectifier with capacitor input filter. Explain the operation with waveforms.
  - (b) A HWR circuit fed a resistive load of  $10K\Omega$  through a power transformer having a step-down turns ratio of 8:1 and operated from 230V, 50Hz A.C. Assume the forward resistance of diode to be  $40\Omega$  and transformer secondary winding resistance as  $12\Omega$ .

Calculate the maximum, RMS and average values of current, DC O/P voltage and power, efficiency of rectification and ripple factor. [16]

- 8. (a) Draw the circuit for darlington pair and derive the expressions for  $A_I$ ,  $A_V$ ,  $R_I$  and  $R_0$ .
  - (b) The figure 4b shows a CE amplifier with collector to base bias. Calculate  $A_I$ ,  $A_V$ ,  $R_I$ . The transistor parameters are  $h_{ie}=1.1$ K,  $h_{fe}=50$ ,  $h_{oe}=25\times 10^{-6}$ A/V,  $h_{re}=2.5\times 10^{-4}$ . [8+8]



 $\mathbf{R05}$ 

### I B.Tech Examinations,June 2011 ELECTRONIC DEVICES AND CIRCUITS Common to BME, IT, ICE, E.COMP.E, ETM, E.CONT.E, EIE, CSE, ECE, CSSE, EEE

Time: 3 hours

Code No: R05010204

Max Marks: 80

### Answer any FIVE Questions All Questions carry equal marks \*\*\*\*

- 1. (a) Draw the drain characteristics of depletion type MOSFET. Explain clearly different operating regions in characteristics with proper reasoning.
  - (b) Describe the construction of a light-emitting diode and explain its operational mechanism. [10+6]
- 2. (a) Classify various oscillators based on O/P waveforms, circuit components, operating frequencies and feedback used.
  - (b) A phase shift oscillator is to be designed with FET having  $g_m = 5000 \mu s$ , rd=4k $\Omega$  while the resistance in the feedback circuit is 9.7k $\Omega$ . Select the proper value of C and  $R_D$  to have the frequency of oscillations as 5KHZ. [10+6]
- 3. (a) When an electron is placed in a magnetic field with a period of rotation  $T = \frac{35.5}{B} \times 10^{-12}$  sec. Show that the trajectory of an electron is a circle.
  - (b) What is the radius described by an electron placed in a magnetic field, perpendicular to its motion, when the accelerating potential is 900v, and  $B = 0.01 wb/m^2$ . What is the time period of rotation? [8+8]
- 4. (a) Draw the circuit diagram of half wave rectifier with capacitor input filter. Explain the operation with waveforms.
  - (b) A HWR circuit fed a resistive load of 10KΩ through a power transformer having a step-down turns ratio of 8:1 and operated from 230V, 50Hz A.C. Assume the forward resistance of diode to be 40Ω and transformer secondary winding resistance as 12Ω.

Calculate the maximum, RMS and average values of current, DC O/P voltage and power, efficiency of rectification and ripple factor. [16]

- 5. (a) i. What is a zener diode? How does it differ from an ordinary pn-junction rectifier diode?
  - ii. Give the V-I characteristics of zener diode and explain its salient features in relation to that of pn diode.
  - iii. Give the equivalent model of zener diode under the reverse biased condition.
  - (b) Using analytical expression for diode current calculate the dynamic slope resistance of a Ge diode at 290<sup>0</sup>k when forward biased at current of 10  $\mu$ A.

[10+6]

### $\mathbf{R05}$

# Set No. 1

- 6. (a) Draw the circuit for darlington pair and derive the expressions for  $A_I$ ,  $A_V$ ,  $R_I$  and  $R_0$ .
  - (b) The figure 4b shows a CE amplifier with collector to base bias. Calculate  $A_I$ ,  $A_V$ ,  $R_I$ . The transistor parameters are  $h_{ie}=1.1$ K,  $h_{fe}=50$ ,  $h_{oe}=25\times 10^{-6}$ A/V,  $h_{re}=2.5\times 10^{-4}$ . [8+8]



7. (a) Define Desensitivity.

Code No: R05010204

- (b) For large values of D, what is  $A_f$ ? What is the significance of this result?
- (c) An Amplifier has a mid-frequency gain of 100 and a bandwidth of 200KHz.
  - i. What will be the new bandwidth and gain if 5% negative feedback is introduced?
  - ii. What should be the amount of negative feedback if the bandwidth is to be restricted to 1MHz? [16]
- 8. (a) What do you understand by Q point? Explain its significance.
  - (b) For the circuit shown (figure3b), calculate the value of stability factor S to make the circuit thermally stable. Assume  $I_{CO}=1$ nA and  $\theta=4.1 \times 10^{8} \ {}^{0}C/W$ . [8+8]



**R05** 

### I B.Tech Examinations,June 2011 ELECTRONIC DEVICES AND CIRCUITS Common to BME, IT, ICE, E.COMP.E, ETM, E.CONT.E, EIE, CSE, ECE, CSSE, EEE

Time: 3 hours

Code No: R05010204

Max Marks: 80

### Answer any FIVE Questions All Questions carry equal marks

\*\*\*\*

- 1. (a) Draw the drain characteristics of depletion type MOSFET. Explain clearly different operating regions in characteristics with proper reasoning.
  - (b) Describe the construction of a light-emitting diode and explain its operational mechanism. [10+6]
- 2. (a) Define Desensitivity.
  - (b) For large values of D, what is  $A_f$ ? What is the significance of this result?
  - (c) An Amplifier has a mid-frequency gain of 100 and a bandwidth of 200KHz.
    - i. What will be the new bandwidth and gain if 5% negative feedback is introduced?
    - ii. What should be the amount of negative feedback if the bandwidth is to be restricted to 1MHz? [16]
- 3. (a) What do you understand by Q point? Explain its significance.
  - (b) For the circuit shown (figure3b), calculate the value of stability factor S to make the circuit thermally stable. Assume  $I_{CO}=1$ nA and  $\theta=4.1 \times 10^{8} \ {}^{0}C/W$ . [8+8]



Figure 3b

### $\mathbf{R05}$

# Set No. 3

- 4. (a) Draw the circuit for darlington pair and derive the expressions for  $A_I$ ,  $A_V$ ,  $R_I$  and  $R_0$ .
  - (b) The figure 4b shows a CE amplifier with collector to base bias. Calculate  $A_I$ ,  $A_V$ ,  $R_I$ . The transistor parameters are  $h_{ie}=1.1$ K,  $h_{fe}=50$ ,  $h_{oe}=25\times 10^{-6}$ A/V,  $h_{re}=2.5\times 10^{-4}$ . [8+8]



- 5. (a) Draw the circuit diagram of half wave rectifier with capacitor input filter. Explain the operation with waveforms.
  - (b) A HWR circuit fed a resistive load of  $10 \text{K}\Omega$  through a power transformer having a step-down turns ratio of 8:1 and operated from 230V, 50Hz A.C. Assume the forward resistance of diode to be  $40\Omega$  and transformer secondary winding resistance as  $12\Omega$ .

Calculate the maximum, RMS and average values of current, DC O/P voltage and power, efficiency of rectification and ripple factor. [16]

- 6. (a) i. What is a zener diode? How does it differ from an ordinary pn-junction rectifier diode?
  - ii. Give the V-I characteristics of zener diode and explain its salient features in relation to that of pn diode.
  - iii. Give the equivalent model of zener diode under the reverse biased condition.
  - (b) Using analytical expression for diode current calculate the dynamic slope resistance of a Ge diode at 290<sup>0</sup>k when forward biased at current of 10  $\mu$ A.

[10+6]

- 7. (a) Classify various oscillators based on O/P waveforms, circuit components, operating frequencies and feedback used.
  - (b) A phase shift oscillator is to be designed with FET having  $g_m = 5000 \mu s$ , rd=4k $\Omega$  while the resistance in the feedback circuit is 9.7k $\Omega$ . Select the proper value of C and  $R_D$  to have the frequency of oscillations as 5KHZ. [10+6]
- 8. (a) When an electron is placed in a magnetic field with a period of rotation  $T = \frac{35.5}{B} \times 10^{-12}$  sec. Show that the trajectory of an electron is a circle.

#### www.firstranker.com

Code No: R05010204

 $\mathbf{R05}$ 

# Set No. 3

(b) What is the radius described by an electron placed in a magnetic field, perpendicular to its motion, when the accelerating potential is 900v, and  $B = 0.01 wb/m^2$ . What is the time period of rotation? [8+8]

\*\*\*\*

RANKER