

Code No: R07A10401

R07**Set No. 2**

I B.Tech Examinations, June 2011
BASIC ELECTRONIC DEVICES AND CIRCUITS
Electrical And Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. (a) Explain the formation of depletion region in an open-circuited p-n junction with neat sketches.
 (b) A p-n junction diode has a reverse saturation current of $30 \mu\text{A}$ at a temperature of 125°C . At the same temperature find the dynamic resistance for 0.2V bias in forward and reverse direction. [8+8]
2. (a) Draw the circuit of a BJT in C.E configuration and explain about the input and output characteristics.
 (b) Derive the relation between α and β . [10+6]
3. Take into account the loading of the RC network in the phase shift oscillator shown in figure 4 If R_0 is the output impedance of the amplifier (assume that C_s is arbitrarily large) prove that the frequency of oscillation f and the minimum gain A are given by [16]

$$f = \frac{1}{2\pi RC} \frac{1}{\sqrt{6+4\left(\frac{R_0}{R}\right)}}$$

$$A = 29 + 23\frac{R_0}{R} + 4\left(\frac{R_0}{R}\right)^2$$

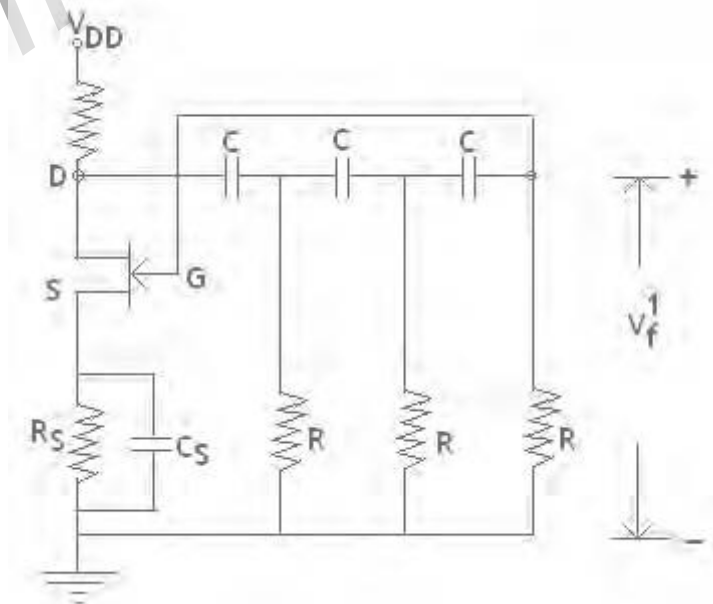


Figure 4

4. (a) What do you understand by dc and ac load line? Explain how to choose the operating point?

Code No: R07A10401

R07**Set No. 2**

- (b) For a fixed bias configuration, determine I_{bQ} , I_{CQ} and V_{ceQ} using the following specifications: $V_{cc}=16V$, $\beta=90$, $R_c=2.7K\Omega$, $R_b=470K\Omega$ and also find the saturation current I_{sat} . [8+8]
5. Show that for the CG amplifier with $R_s=0$ and $C_{ds}=0$

$$y_i = g_m + g_d(1 - A_V) + j\omega C_{gs}$$
 [16]
6. (a) Discuss the operation of a FW rectifier with and without capacitor filter.
 (b) Calculate the magnitude of the ripple factor for the given set of observations of $V_{ac}=24.2$ volts and $V_{DC}=20$ volts. Identify the type of rectifier circuit based on the knowledge of theoretical values of ripple factors for Half wave and Full wave rectifier circuits. [8+8]
7. (a) With the help of a block schematic, explain the working of a CRO and what are the applications of CRO?
 (b) In a CRT, a pair of deflecting plates are 2.5 cm long and 0.5 cm apart. The distance from the centre of the plates to the screen is 20 cm. The final anode voltage is 1200V. Calculate:
 i. The displacement produced for a deflecting voltage of 20V
 ii. The angle, which the beam makes with the axis of the tube on emerging from the field. [10+6]
8. (a) Define Desensitivity D. What is the significance of this?
 (b) An amplifier without feedback gives a fundamental output of 36V with 7 percent second-harmonic distortion when the input is 0.028V. If 1.2 percent of the output is fed back into the input in a negative voltage series feedback circuit, what is the output voltage? If the fundamental output is maintained at 36V but the second-harmonic distortion is reduced to 1 percent, what is the input voltage? [6+10]

Code No: R07A10401

R07**Set No. 4**

I B.Tech Examinations, June 2011
BASIC ELECTRONIC DEVICES AND CIRCUITS
Electrical And Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. (a) Define Desensitivity D. What is the significance of this?
 (b) An amplifier without feedback gives a fundamental output of 36V with 7 percent second-harmonic distortion when the input is 0.028V. If 1.2 percent of the output is fed back into the input in a negative voltage series feedback circuit, what is the output voltage? If the fundamental output is maintained at 36V but the second-harmonic distortion is reduced to 1 percent, what is the input voltage? [6+10]
2. Take into account the loading of the RC network in the phase shift oscillator shown in figure 4. If R_0 is the output impedance of the amplifier (assume that C_s is arbitrarily large) prove that the frequency of oscillation f and the minimum gain A are given by [16]

$$f = \frac{1}{2\pi RC} \frac{1}{\sqrt{6+4\left(\frac{R_0}{R}\right)}}$$

$$A = 29 + 23\frac{R_0}{R} + 4\left(\frac{R_0}{R}\right)^2$$

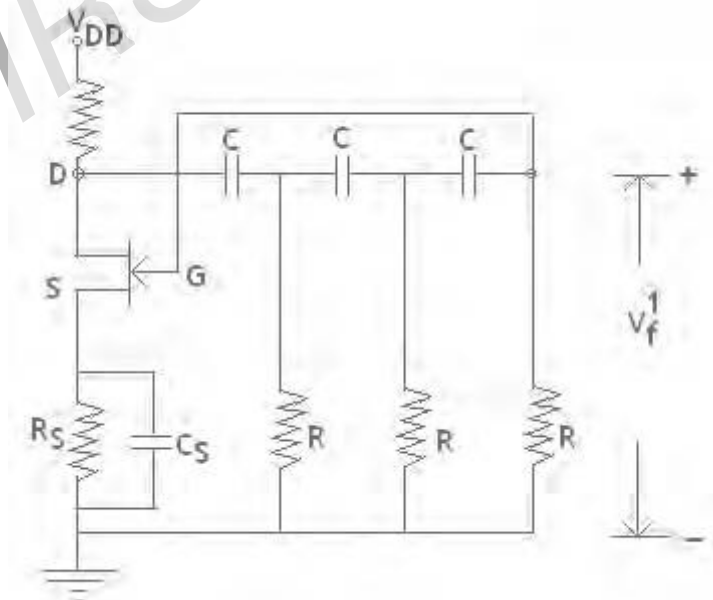


Figure 4

3. (a) Explain the formation of depletion region in an open-circuited p-n junction with neat sketches.

Code No: R07A10401

R07

Set No. 4

- (b) A p-n junction diode has a reverse saturation current of $30 \mu\text{A}$ at a temperature of 125°C . At the same temperature find the dynamic resistance for 0.2V bias in forward and reverse direction. [8+8]
4. (a) Draw the circuit of a BJT in C.E configuration and explain about the input and output characteristics.
- (b) Derive the relation between α and β . [10+6]
5. (a) Discuss the operation of a FW rectifier with and without capacitor filter.
- (b) Calculate the magnitude of the ripple factor for the given set of observations of $V_{ac} = 24.2\text{volts}$ and $V_{DC} = 20\text{ volts}$. Identify the type of rectifier circuit based on the knowledge of theoretical values of ripple factors for Half wave and Full wave rectifier circuits. [8+8]
6. (a) What do you understand by dc and ac load line? Explain how to choose the operating point?
- (b) For a fixed bias configuration, determine I_{bQ} , I_{CQ} and V_{ceQ} using the following specifications: $V_{cc} = 16\text{V}$, $\beta = 90$, $R_c = 2.7\text{K}\Omega$, $R_b = 470\text{K}\Omega$ and also find the saturation current I_{sat} . [8+8]
7. Show that for the CG amplifier with $R_s = 0$ and $C_{ds} = 0$
- $$y_i = g_m + g_d(1 - A_V) + j\omega C_{gs} \quad [16]$$
8. (a) With the help of a block schematic, explain the working of a CRO and what are the applications of CRO?
- (b) In a CRT, a pair of deflecting plates are 2.5 cm long and 0.5 cm apart. The distance from the centre of the plates to the screen is 20 cm . The final anode voltage is 1200V . Calculate:
- The displacement produced for a deflecting voltage of 20V
 - The angle, which the beam makes with the axis of the tube on emerging from the field. [10+6]

Code No: R07A10401

R07**Set No. 1**

I B.Tech Examinations, June 2011
BASIC ELECTRONIC DEVICES AND CIRCUITS
Electrical And Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. (a) Define Desensitivity D. What is the significance of this?
 (b) An amplifier without feedback gives a fundamental output of 36V with 7 percent second-harmonic distortion when the input is 0.028V. If 1.2 percent of the output is fed back into the input in a negative voltage series feedback circuit, what is the output voltage? If the fundamental output is maintained at 36V but the second-harmonic distortion is reduced to 1 percent, what is the input voltage? [6+10]
2. (a) Discuss the operation of a FW rectifier with and without capacitor filter.
 (b) Calculate the magnitude of the ripple factor for the given set of observations of $V_{ac} = 24.2$ volts and $V_{DC} = 20$ volts. Identify the type of rectifier circuit based on the knowledge of theoretical values of ripple factors for Half wave and Full wave rectifier circuits. [8+8]
3. (a) With the help of a block schematic, explain the working of a CRO and what are the applications of CRO?
 (b) In a CRT, a pair of deflecting plates are 2.5 cm long and 0.5 cm apart. The distance from the centre of the plates to the screen is 20 cm. The final anode voltage is 1200V. Calculate:
 - i. The displacement produced for a deflecting voltage of 20V
 - ii. The angle, which the beam makes with the axis of the tube on emerging from the field. [10+6]
4. Show that for the CG amplifier with $R_s = 0$ and $C_{ds} = 0$

$$y_i = g_m + g_d(1 - A_V) + j\omega C_{gs}$$
 [16]
5. (a) What do you understand by dc and ac load line? Explain how to choose the operating point?
 (b) For a fixed bias configuration, determine I_{bQ} , I_{cQ} and V_{ceQ} using the following specifications: $V_{cc} = 16V$, $\beta = 90$, $R_c = 2.7K\Omega$, $R_b = 470K\Omega$ and also find the saturation current I_{sat} . [8+8]
6. (a) Explain the formation of depletion region in an open-circuited p-n junction with neat sketches.
 (b) A p-n junction diode has a reverse saturation current of $30 \mu A$ at a temperature of $125^\circ C$. At the same temperature find the dynamic resistance for 0.2V bias in forward and reverse direction. [8+8]

Code No: R07A10401

R07

Set No. 1

7. (a) Draw the circuit of a BJT in C.E configuration and explain about the input and output characteristics.
 (b) Derive the relation between α and β . [10+6]
8. Take into account the loading of the RC network in the phase shift oscillator shown in figure 4 If R_0 is the output impedance of the amplifier (assume that C_s is arbitrarily large) prove that the frequency of oscillation f and the minimum gain A are given by [16]

$$f = \frac{1}{2\pi RC} \frac{1}{\sqrt{6+4\left(\frac{R_0}{R}\right)}}$$

$$A = 29 + 23\frac{R_0}{R} + 4\left(\frac{R_0}{R}\right)^2$$

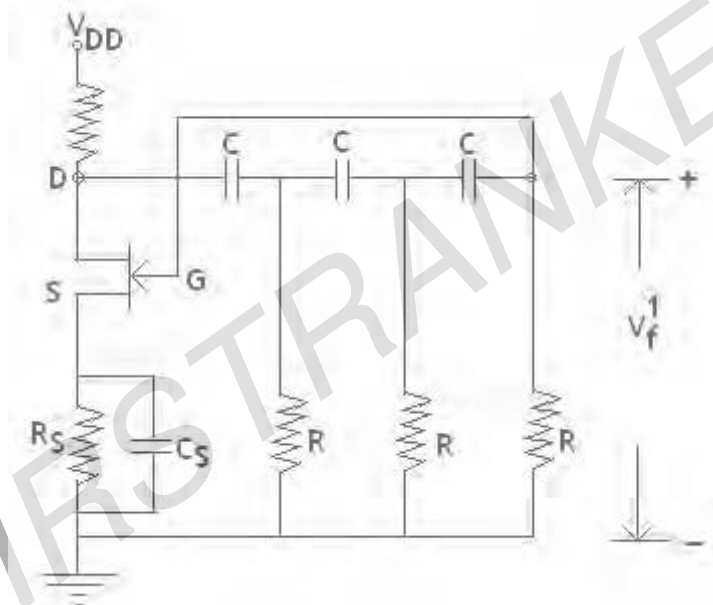


Figure 4

Code No: R07A10401

R07**Set No. 3**

I B.Tech Examinations, June 2011
BASIC ELECTRONIC DEVICES AND CIRCUITS
Electrical And Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. (a) With the help of a block schematic, explain the working of a CRO and what are the applications of CRO?
- (b) In a CRT, a pair of deflecting plates are 2.5 cm long and 0.5 cm apart. The distance from the centre of the plates to the screen is 20 cm. The final anode voltage is 1200V. Calculate:
 - i. The displacement produced for a deflecting voltage of 20V
 - ii. The angle, which the beam makes with the axis of the tube on emerging from the field. [10+6]
2. Show that for the CG amplifier with $R_s=0$ and $C_{ds}=0$

$$y_i = g_m + g_d(1 - A_V) + j\omega C_{gs}$$
[16]
3. (a) Define Desensitivity D. What is the significance of this?
- (b) An amplifier without feedback gives a fundamental output of 36V with 7 percent second-harmonic distortion when the input is 0.028V. If 1.2 percent of the output is fed back into the input in a negative voltage series feedback circuit, what is the output voltage? If the fundamental output is maintained at 36V but the second-harmonic distortion is reduced to 1 percent, what is the input voltage? [6+10]
4. Take into account the loading of the RC network in the phase shift oscillator shown in figure 4 If R_0 is the output impedance of the amplifier (assume that C_s is arbitrarily large) prove that the frequency of oscillation f and the minimum gain A are given by [16]

$$f = \frac{1}{2\pi RC} \frac{1}{\sqrt{6+4\left(\frac{R_o}{R}\right)}}$$

$$A = 29 + 23\frac{R_o}{R} + 4\left(\frac{R_o}{R}\right)^2$$

Code No: R07A10401

R07

Set No. 3

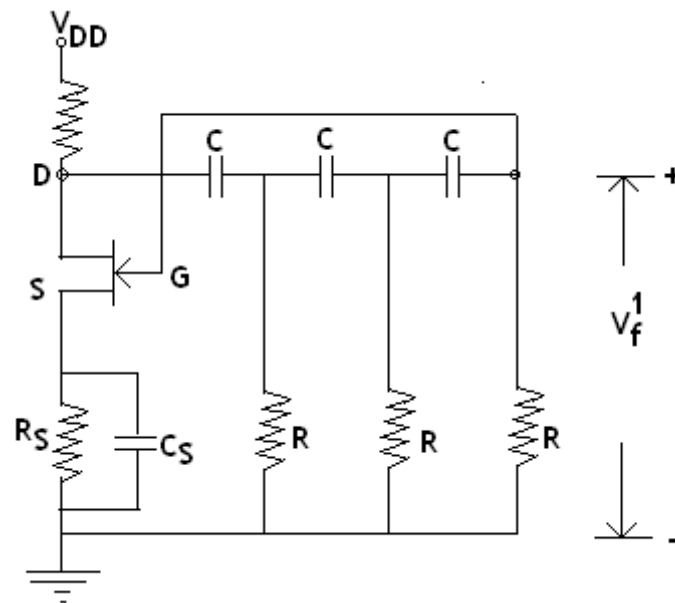


Figure 4

5. (a) Discuss the operation of a FW rectifier with and without capacitor filter.
 (b) Calculate the magnitude of the ripple factor for the given set of observations of $V_{ac} = 24.2$ volts and $V_{DC} = 20$ volts. Identify the type of rectifier circuit based on the knowledge of theoretical values of ripple factors for Half wave and Full wave rectifier circuits. [8+8]
6. (a) What do you understand by dc and ac load line? Explain how to choose the operating point?
 (b) For a fixed bias configuration, determine I_{bQ} , I_{CQ} and V_{ceQ} using the following specifications: $V_{cc} = 16V$, $\beta = 90$, $R_c = 2.7K\Omega$, $R_b = 470K\Omega$ and also find the saturation current I_{sat} . [8+8]
7. (a) Explain the formation of depletion region in an open-circuited p-n junction with neat sketches.
 (b) A p-n junction diode has a reverse saturation current of $30 \mu A$ at a temperature of $125^\circ C$. At the same temperature find the dynamic resistance for $0.2V$ bias in forward and reverse direction. [8+8]
8. (a) Draw the circuit of a BJT in C.E configuration and explain about the input and output characteristics.
 (b) Derive the relation between α and β . [10+6]
