

Code No: R07A1EC05

R07**Set No. 2**

I B.Tech Examinations, June 2011

NETWORK ANALYSIS

Common to BME, E.COMP.E, ETM, E.CONT.E, EIE, ECE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions

All Questions carry equal marks

1. A network has two branches in parallel. The branch 'a' has a $5\ \Omega$ resistance and $15\ \Omega$ capacitive reactance in series. The branch 'b' has $10\ \Omega$ resistance and $12\ \Omega$ inductive reactance in series. It is fed from 100V , $50\ \text{Hz}$ supply. Find
 - (a) Branch currents.
 - (b) Circuit current
 - (c) Power factor of the circuit
 - (d) Total active power. [16]
2. Design a T-type and π -type attenuator if the characteristic resistance is $200\ \Omega$ and the attenuation is 200dB . [16]
3. For the figure 1 shown, calculate the equivalent resistance of the following combination of resistors and also calculate the source current, total power dissipated. [16]

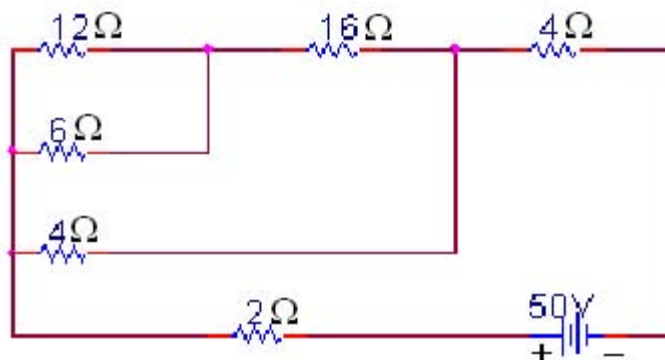


Figure 1:

4. A series RLC circuit with $R = 50\ \Omega$, $L = 0.1\ \text{H}$ and $C = 50\ \mu\text{F}$ has a constant voltage, $V = 100\ \text{volts}$ applied at $t = 0$. Find the current transient assuming zero initial charge on the capacitor. [16]
5. State, explain and prove Reciprocity Theorem. [16]
6. A symmetrical 3 phase, $400\ \text{V}$ system supplies a balanced mesh connected load. The current in each branch circuit is $20\ \text{A}$ and the phase angle is $40\ \text{deg}$ lag. Find

Code No: R07A1EC05

R07**Set No. 2**

(a) the line current

(b) the total power.

[16]

7. Calculate the Y - parameters of the circuit as shown in fig. 3 and draw the corresponding equivalent circuit. [16]

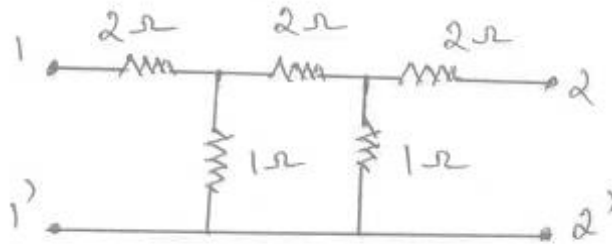


Figure 3

8. For the network shown in figure 2, draw the oriented graph, select a tree and obtain a tie-set matrix. Write down the KVL equations from the tie-set matrix. [16]

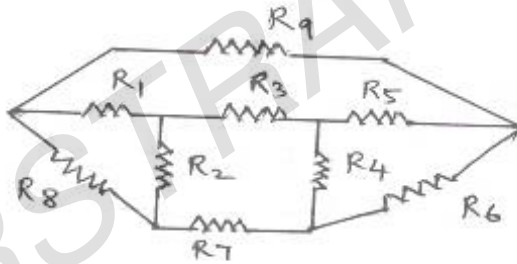


Figure 2

Code No: R07A1EC05

R07**Set No. 4**

I B.Tech Examinations, June 2011

NETWORK ANALYSIS

Common to BME, E.COMP.E, ETM, E.CONT.E, EIE, ECE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions

All Questions carry equal marks

1. A network has two branches in parallel. The branch 'a' has a $5\ \Omega$ resistance and $15\ \Omega$ capacitive reactance in series. The branch 'b' has $10\ \Omega$ resistance and $12\ \Omega$ inductive reactance in series. It is fed from 100V , $50\ \text{Hz}$ supply. Find
- Branch currents.
 - Circuit current
 - Power factor of the circuit
 - Total active power.
- [16]
2. For the figure 2 shown, calculate the equivalent resistance of the following combination of resistors and also calculate the source current, total power dissipated.
- [16]

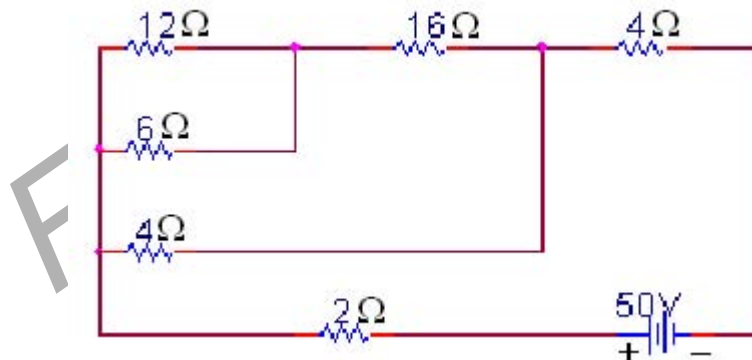


Figure 2:

3. For the network shown in figure 3, draw the oriented graph, select a tree and obtain a tie-set matrix. Write down the KVL equations from the tie-set matrix.
- [16]

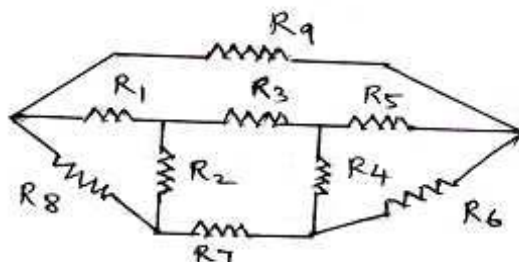


Figure 3

Code No: R07A1EC05

R07**Set No. 4**

4. Calculate the Y - parameters of the circuit as shown in fig. 4 and draw the corresponding equivalent circuit. [16]

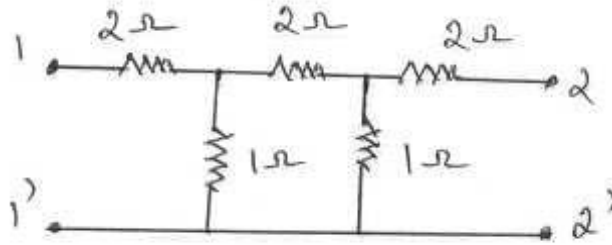


Figure 4

5. State, explain and prove Reciprocity Theorem. [16]
6. A symmetrical 3 phase, 400 V system supplies a balanced mesh connected load. The current in each branch circuit is 20A and the phase angle is 40 deg lag. Find
 (a) the line current
 (b) the total power. [16]
7. Design a T-type and π -type attenuator if the characteristic resistance is 200Ω and the attenuation is 200dB. [16]
8. A series RLC circuit with $R = 50\Omega$, $L = 0.1$ H and $C = 50\mu\text{F}$ has a constant voltage, $V = 100$ volts applied at $t = 0$. Find the current transient assuming zero initial charge on the capacitor. [16]

Code No: R07A1EC05

R07**Set No. 1**

I B.Tech Examinations, June 2011

NETWORK ANALYSIS

Common to BME, E.COMP.E, ETM, E.CONT.E, EIE, ECE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. Calculate the Y - parameters of the circuit as shown in fig. 1 and draw the corresponding equivalent circuit. [16]

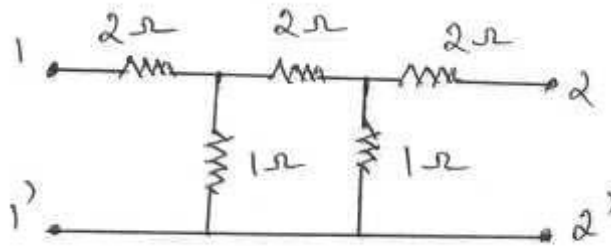


Figure 1

2. For the network shown in figure 2, draw the oriented graph, select a tree and obtain a tie-set matrix. Write down the KVL equations from the tie-set matrix. [16]

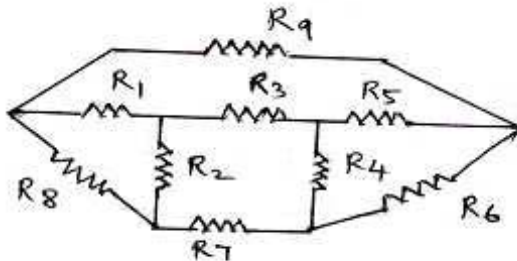


Figure 2

3. A series RLC circuit with $R = 50\Omega$, $L = 0.1 \text{ H}$ and $C = 50\mu\text{F}$ has a constant voltage, $V = 100 \text{ volts}$ applied at $t = 0$. Find the current transient assuming zero initial charge on the capacitor. [16]
4. A symmetrical 3 phase, 400 V system supplies a balanced mesh connected load. The current in each branch circuit is 20A and the phase angle is 40 deg lag. Find
- the line current
 - the total power. [16]
5. State, explain and prove Reciprocity Theorem. [16]
6. For the figure 3 shown, calculate the equivalent resistance of the following combination of resistors and also calculate the source current, total power dissipated. [16]

Code No: R07A1EC05

R07

Set No. 1

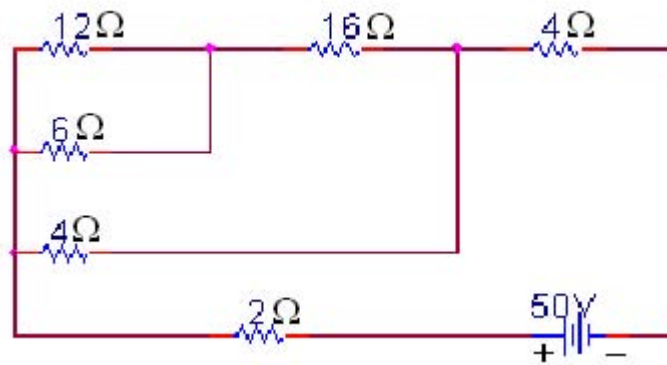


Figure 3:

7. Design a T-type and π -type attenuator if the characteristic resistance is 200Ω and the attenuation is 200dB. [16]
8. A network has two branches in parallel. The branch 'a' has a 5Ω resistance and 15Ω capacitive reactance in series. The branch 'b' has 10Ω resistance and 12Ω inductive reactance in series. It is fed from 100V, 50 Hz supply. Find
- Branch currents.
 - Circuit current
 - Power factor of the circuit
 - Total active power. [16]

Code No: R07A1EC05

R07**Set No. 3**

I B.Tech Examinations, June 2011

NETWORK ANALYSIS

Common to BME, E.COMP.E, ETM, E.CONT.E, EIE, ECE

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions

All Questions carry equal marks

- Design a T-type and π -type attenuator if the characteristic resistance is 200Ω and the attenuation is 200dB. [16]
- For the network shown in figure 2, draw the oriented graph, select a tree and obtain a tie-set matrix. Write down the KVL equations from the tie-set matrix. [16]

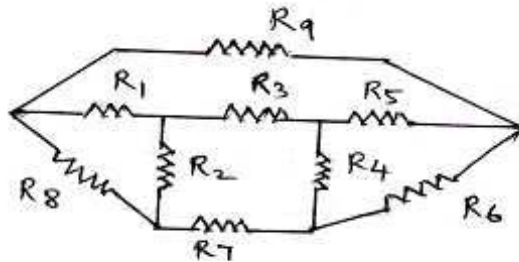


Figure 2

- Calculate the Y - parameters of the circuit as shown in fig. 3 and draw the corresponding equivalent circuit. [16]

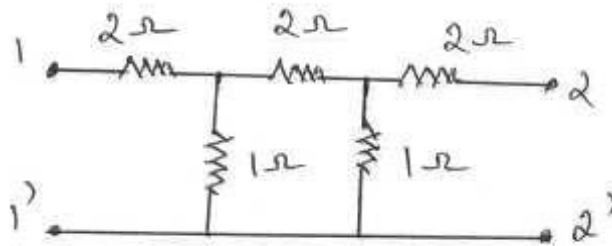


Figure 3

- For the figure 4 shown, calculate the equivalent resistance of the following combination of resistors and also calculate the source current, total power dissipated. [16]
- A series RLC circuit with $R = 50\Omega$, $L = 0.1$ H and $C = 50\mu\text{F}$ has a constant voltage, $V = 100$ volts applied at $t = 0$. Find the current transient assuming zero initial charge on the capacitor. [16]
- A network has two branches in parallel. The branch 'a' has a 5Ω resistance and 15Ω capacitive reactance in series. The branch 'b' has 10Ω resistance and 12Ω inductive reactance in series. It is fed from 100V, 50 Hz supply. Find

Code No: R07A1EC05

R07

Set No. 3

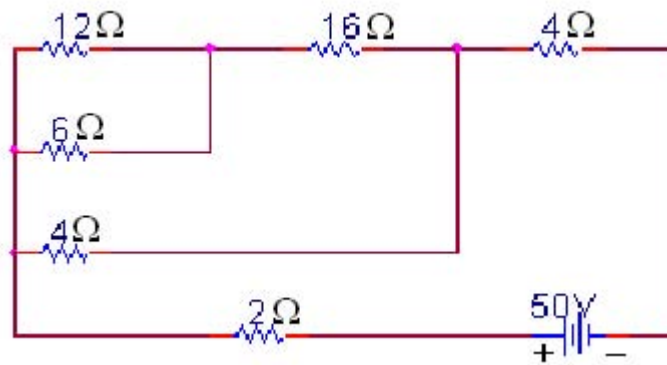


Figure 4:

- (a) Branch currents.
 (b) Circuit current
 (c) Power factor of the circuit
 (d) Total active power. [16]
7. State, explain and prove Reciprocity Theorem. [16]
8. A symmetrical 3 phase, 400 V system supplies a balanced mesh connected load. The current in each branch circuit is 20A and the phase angle is 40 deg lag. Find
 (a) the line current
 (b) the total power. [16]
