

Code No: D0608

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**  
**M.Tech II - Semester Examinations, March/April 2011**  
**CMOS ANALOG AND MIXED SIGNAL DESIGN**  
**(DIGITAL SYSTEMS AND COMPUTER ELECTRONICS)**

Time: 3hours

Max. Marks: 60

**Answer any five questions**  
**All questions carry equal marks**

- - -

- 1) a) Explain how layout techniques improve the matching in MOSFET mirrors?  
 b) Derive the expression for sensitivity of  $I_0$  due to  $V_{dd}$ , temperature coefficient TC of  $I_0$ . [12]
- 2) a) Draw the circuit of a Beta multiplier referred self biasing circuit and derive the expression for temperature coefficient.  
 b) Using the Beta multiplier current reference, design a  $10\mu A$  current source. Estimate the temperature coefficient and assume  $V_{dd} = -V_{ss} = 2.5v$ . [12]
- 3) a) Explain two different types of gate drain connected load amplifiers.  
 b) Draw the circuit of a shunt-shunt feedback amplifier and explain its working along with parameter calculations. [12]
- 4) a) Explain the operation of a wide swing differential amplifier.  
 b) Design a two stage CMOS OPAMP with the following specifications  $A_0=55000$ ,  $GBW=1.2MHz$ ,  $SR=2.5V/\mu sec$ . [12]
- 5) a) Explain the design and analysis of a Tran conductance amplifier..  
 b) Draw the circuit for cross coupled pair differential amplifier with active loads and derive the expression for  $A_v$ . [12]
- 6) a) Explain dynamic comparator and dynamic biasing of current mirror circuits.  
 b) Find the device dimensions of the input stage for a 2-stage comparator to meet the following specifications. Input common Mode Range is 1.5 v to 9v,  $V_{dd}=10v$ ,  $V_{ss}= 0v$ . [12]
- 7) a) Design a Zero temperature coefficient voltage Beat Multiplier reference at  $300^0k$  with  $V_{ss}= 0v$  and  $V_{dd}=5v$ . Determine the sensitivity for changing  $V_{dd}$  and Temperature T.  
 b) Explain the basic building blocks of a switched capacitor circuit. [12]
- 8) a) Design a bit current steering DAC using the generic current steering DAC. Assume that each current I is 5 mA and find the total output current for each input node.  
 b) Explain different characteristics Parameters of ADC and DACS. [12]

\*\*\*\*\*