

Code No: C8802

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

M.Tech I Semester Examinations, March/April 2011

SIGNAL CONDITIONING CIRCUITS
(ELECTRONICS AND INSTRUMENTATION)

Time: 3hours

Max. Marks: 60

Answer any five questions
All questions carry equal marks

- - -

1. Design a Practical differentiator to differentiate an input signal that varies in frequency from 20 Hz to 1 K Hz.
 - (a) If a sine wave of 1V peak at 1000 Hz is applied to the above differentiator, draw its output wave form.
 - (b) If a square wave of 1V peak at 500 Hz is applied to the above differentiator, draw its output wave form. [8+2+2]
2. (a) Calculate upper and lower cutoff frequencies for a Band Pass active filter with $R_1=R_2=10\text{Kohms}$, $R_{f1}=R_{f2}=100\text{Kohms}$, $R_L=R_H=10\text{Kohms}$, $C_L=1\mu\text{F}$ & $C_H=1\text{ pF}$.
(b) Draw operational amplifier in conjunction with capacitance Transducers and derive relation for output voltage. [8+4]
3. An analog transducer with a 0-10V input is able to distinguish a change of 10mv in its input signal.
 - (a) Calculate its resolution.
 - (b) Calculate no of bits of an ADC so that the digital output has almost the same resolution as the above transducer.
 - (c) Calculate also Quantization error.
 - (d) No of decision levels and comment on results. [3+2+3+4]
4. (a) Construct the circuit of instrumentation amplifier using 3 op-amp's and explain in detail.
(b) Derive the relation for each op-amp output voltage in an instrumentation amplifier. [6+6]
5. Explain the principle of operation of the following
 - (a) Carrier amplifier
 - (b) Variable Oscillator. [6+6]
6. (a) Explain Charge amplifiers with sketch.
(b) Explain the working Chopper and low drift amplifiers [6+6]
7. (a) Explain Signal conditioning circuits for push pull type transducers.
(b) Explain direct digital converter [6+6]
8. (a) Explain briefly Data acquisition system with block diagram.
(b) Explain the need of Microprocessors and Microcontrollers for signal conditioning. [8+4]

* * * * *