

II B.TECH - II SEMESTER EXAMINATIONS, APRIL/MAY, 2011 NETWORK THEORY

(ELECTRICAL AND ELECTRONICS ENGINEERING)

Time: 3hours

Answer any FIVE questions All Questions Carry Equal Marks

Max. Marks: 75

- 1.a) Derive the expression for the power measured and power factor in the two watt meter method applied for balanced loads.
 - b) A 3-phase 500 V motor operates at a power factor of 0.4 and takes an input power of 30 kW. Two watt meters are employed to measure the input power. Find readings on each instrument. [7+8]
- 2.a) The circuit shown in the figure 1 has no stored energy. Find the Laplace transform of current supplied by the battery up on the closure of switch at t = 0. Hence find the initial and final values of the current.



- b) Explain the procedure adopted for the evaluation of initial conditions. [8+7]
- 3.a) Derive expression for the transient response of an R L series circuit excited by sinusoidal excitation.
- b) A series R C circuit with $R = 100 \Omega$ and $C = 25 \mu F$ has a sinusoidal excitation V(t) = 250 Sin 500t. Find the total current assuming that the capacitor is initially uncharged. [7+8]
- 4.a) Find the transform impedance of the network shown in below figure 2.
- b) What is a transfer function? Explain the necessary conditions for transfer functions.

[8+7]



b)

CODE NO: R09220205



SET No - 1

5.a) For the circuit shown in the figure 3 find Z and Y parameters.

Express Y – parameters in terms of h – parameters.



Figure 3

[8+7]

[15]

6. Find the Y – parameters and ABCD parameters for the following network (figure 4).



- 7.a) Explain the general configuration and parameters of a constant K low pass filter T and π Sections.
 - b) Design a constant K T-Section and π section low pass filter having cut off frequency $f_c = 2kHz$ and normal impedance $Z0 = 600 \Omega$. [7+8]
- 8.a) Determine the function f(t) if the Fourier Transform of the function is

(jw) =
$$A e^{j\pi/2}$$
 $-w_0 < w < 0$
 $A e^{-j\pi/2}$ $0 < w < w_0$

F

b) Determine the Fourier series of the wave form shown in figure 5using Trigonometric series. [7+8]





II B.TECH - II SEMESTER EXAMINATIONS, APRIL/MAY, 2011 NETWORK THEORY

(ELECTRICAL AND ELECTRONICS ENGINEERING)

Time: 3hours

Answer any FIVE questions All Questions Carry Equal Marks

- Max. Marks: 75
- 1.a) Derive expression for the power measured in two watt meter method for un balanced loads.
 - b) The two watt meter readings in a 3 phase power measurement are 800 W and 400 W. The latter reading is being obtained after the reversal of current coil. Calculate the total power and power factor of the load. [7+8]
- 2.a) A current source of the figure 1 shown below supplies at current

ilb

$$i(t) = 0, t \le 0$$

 $i(t) = t, t > 0.$

Find $V_0(t)$

b) Derive the expression for the transient response of RC series circuit excited by a dc voltage source. Use Laplace technique. [8+7]

Volt)

- 3.a) Derive the expression for the transient response of an RLC series circuit excited by a Sinusoidal source.
 - b) A Sinusoidal Voltage of 12 sin 8 t Volts is applied at t = 0 to a RC series of $R = 4\Omega$ and L = 1 H. By Laplace transform method determine the circuit current i (t) for $t \ge 0$. Assume zero initial condition. [7+8]
- 4.a) Explain the necessary conditions for driving point functions.

b) Find the transform impedance of the following circuit (figure 2). [8+7] $_{2}H$ $_{4}\Omega$



Figure 2



[7+8]

- 5.a) Express ABCD parameters in terms of h – parameters. **b**) Determine Y – parameters of the network shown in figure 3. [8+7] 100-2 40~ V ₹200-∿ 00 Ź5 11 Figure 3 [15] 6. For the network shown in the figure 4. Find Y and Z – parameters. 14 5-~ V_2 24 ۱. 11 Figure 4
- 7.a) What is high pass filter? Explain the general configuration and parameters of a constant K high pass filter.
 - b) Design a constant K T section and π section high pan filters having cut off frequency $f_c = 10$ KHz and characteristic impedance $Z_0 = 600 \Omega$. Also find the characteristic impedance at 25 KHz. [7+8]
- 8.a) What is Fourier transform? What are its properties?
 - b) Find the Fourier transform of the triangular wave shown in the figure 5 given below.

 $-a_{12}$ Figure 5 $f^{(e)}$ v_{0} a_{12} t

www.firstranker.com





II B.TECH - II SEMESTER EXAMINATIONS, APRIL/MAY, 2011 NETWORK THEORY

(ELECTRICAL AND ELECTRONICS ENGINEERING)

Time: 3hours

Answer any FIVE questions

Max. Marks: 75

All Questions Carry Equal Marks

- 1.a) Discuss the effect of variation of power factor on the readings of two watt meters used in 3-phase power measurement.
 - b) Calculate the active and reactive components of the currents in each phase of a star connected generator supplying at 11 kV to a load of 5 MW at 0.8 pf lagging. What is the value of new output if the total current is same and the pf is raised to 0.85? [7+8]
- 2.a) Derive the expressions for the transient current of RL series circuit when excited by a dc voltage.
 - b) The network shown in figure 1 the switch in position 1 at t = 0 and after 200 ms it is moved to position 2. What is the expression for the current flowing through the capacitor? [7+8]



- 3.a) Derive expression for transient response of RC series circuit excited by a sinusoidal source.
 - b) A series RL circuit with R = 50 ohms and L = 0.2 H has a sinusoidal voltage source $V = 150 \ Sin(500t + \phi)$ volts applied at a time when $\phi = 0$. Find the expression for the total current. Use Laplace transforms method. [7+8]
- 4.a) What is a transfer function? What are the properties of a transfer function?
- b) What are poles and zeros? Explain their significance.
- c) Draw the pole-zero plots for a system with following network function.

$$Z(s) = \frac{\left(s^3 + 2s^2 + 3s + 2\right)}{s^4 + 6s^3 + 8s^2}.$$
 [4+4+7]

- 5.a) Express Y-Parameter in terms of ABCD parameters.
- b) Find the h-parameters for the following network shown in figure 2. [7+8]



R09

6. For the following network shown in figure 3 determine h-parameters and ABCD parameters. [15]



- 7.a) What is an m-derived filter? Explain the general configuration and parameters of mderived low pass filter for T and Π-Sections.
 - b) Design an m derived high pass Π-Section filter having a cut off frequency 3250 Hz. The frequency of infinite attenuation may be taken at 2750 Hz. The characteristic impedance is 450Ω.
- 8.a) State and explain Fourier Theorem.
- b) The sweep voltage wave form is shown in the figure 4 given below. Find the exponential form of the Fourier series. Draw the frequency and phase spectrums. [7+8]





Max. Marks: 75

II B.TECH - II SEMESTER EXAMINATIONS, APRIL/MAY, 2011 NETWORK THEORY

(ELECTRICAL AND ELECTRONICS ENGINEERING)

Time: 3hours

Answer any FIVE questions

All Questions Carry Equal Marks

- 1.a) Explain the measurement of reactive power in a 3-phase circuit single wattmeter method.
 - b) A balanced 3-phase star connected load of 200 kW takes a leading current of 150 amps with a line voltage of 1200 V at 60 Hz. What are the circuit constants of the load per phase?
- 2.a) Derive the expression for the transient response in an RLC series circuit excited by a DC source.
 - b) A constant voltage is applied to a series RL circuit at t = 0. The voltage across the inductor at t = 3.46 ms is 20 V and 5 V at t = 25 ms. Obtain R if L = 2H. [7+8]
- 3.a) A series RLC circuit with R = 10 Ω , L = 0.1 H and C = 2 μ F is excited by a source with v(t) = 200 $Cos(250t + \Pi/4)$. Determine the complete solution for the current when the circuit is closed at t = 0.
 - b) Derive the expression for the transient response of RC series circuit excited by a sinusoidal excitation. Use Laplace transform approach. [7+8]
- 4.a) How can you assess the nature of time domain response from pole-zero plot? Explain.
- b) Find the transform impedance of the following circuit shown in figure 1. [7+8]



Figure 1

- 5.a) Find the relationship between z and h parameters.
 - b) For the following network shown in figure 2 determine Y parameters.

[7+8]





SET No - 4

6. For the following network shown in figure 3 determine Y and Z parameters. [15]





- 7.a) What is a band pass filter? Explain the general configuration and various parameters of constant-k band pass filters for T and Π-Sections.
- b) What are the steps involved in design of composite filter?
- 8.a) Find the exponential form of the Fourier Series expansion for the periodic rectangular pulse train shown in figure 4. Also draw frequency spectrum taking $\frac{T_p}{T} = \frac{1}{2}$.



[8+7]

[7+8]

b) What are the properties of Fourier Transform?