

www.FirstRanker.com

Enrolment No. www.FirstRanker.com

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER- IV EXAMINATION - SUMMER 2020

Subject Code: 2141004

Date:29/10/2020

Subject Name: CONTROL SYSTEM ENGINEERING

Time: 10:30 AM TO 01:00 PM

Total Marks: 70

Instructions:

c.

c.

Q.2 a.

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Draw the equivalent mechanical system for the system shown in figure 1. 3 Q.1 a. Also write the set of equilibrium equations for it.







Obtain the block diagram for the electrical network shown in figure 3. с.

7

4

3

4

7



- b. Define the following with respect to Bode Plot:
 - 1. Gain cross over frequency
 - 2. Phase cross over frequency
 - 3. Gain Margin
 - 4. Phase Margin
 - c. Write a short note on state space representation of a control system.

4

7

www.FirstRanker.com